



In wire-based designs, all components are connected with wire lines crossing over each other. When a design has numerous components, these overlapping lines make it impossible to cross-check and adhere to design rules. However, with nets, each net port and pin connection can be clearly cross-checked to see which pins and how many components are connected.

For instance, if you have a voltage regulator IC powering the main chip, sensors, indication system, and clock signal generator in a system, selecting the output pin on the power system circuit shows all other components connected to it. If you want to replace the regulator in a later version or make modifications, you can easily modify the power system module, and all other circuits adapt to that new IC of the voltage regulator. You only need to manage the name of the net port for that. **EFY**

Fig. 5: Cross-checking in wire-based design vs checking the design connection using nets

ELECTRONICS FOR YOU | APRIL 2024 **85**