

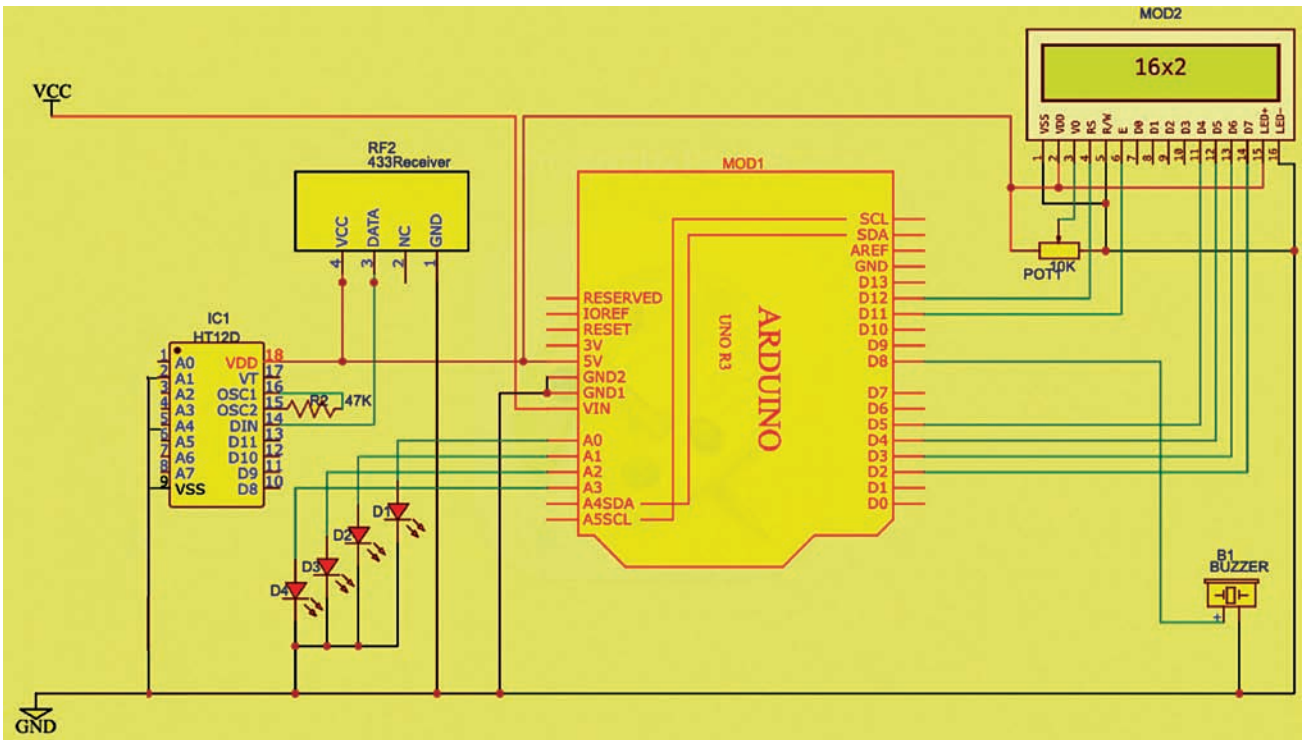


Fig. 2: Receiver circuit with LCD

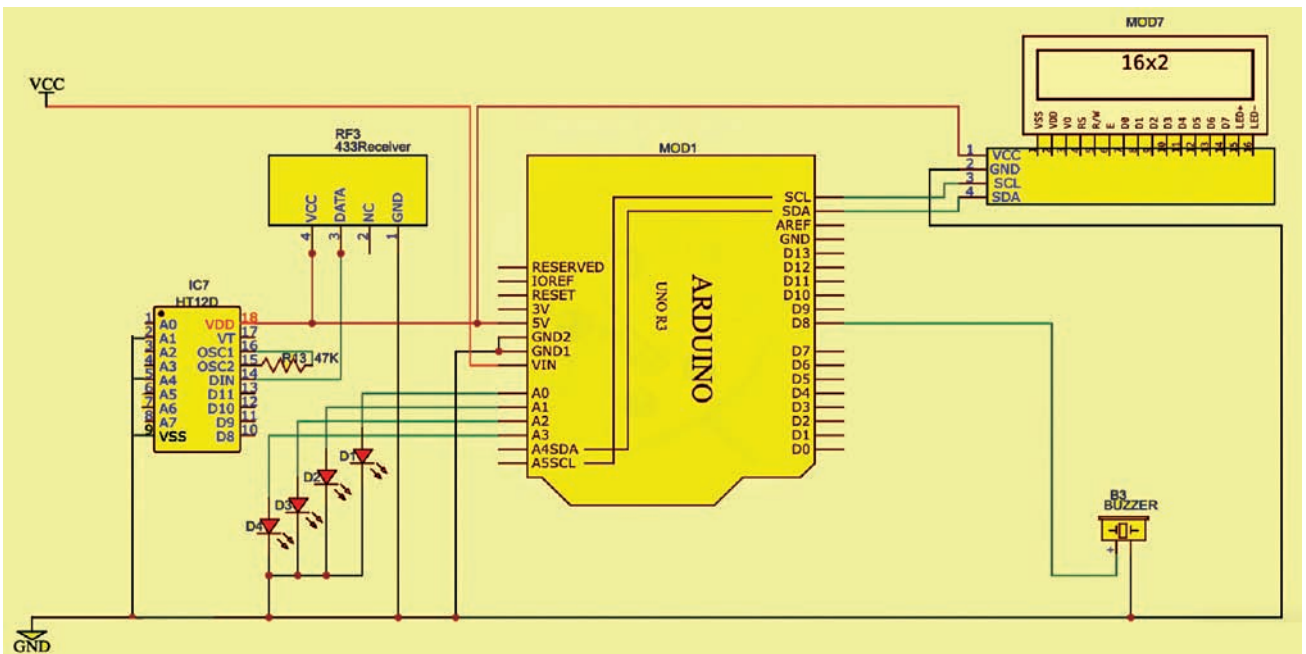


Fig. 3: Receiver circuit with I2C display

allow customers to place orders directly to the manager or the kitchen.

The list of components required is detailed in the table.

Circuit and working

The device consists of two main sections: the transmitter and the receiver. Their operations are

outlined below.

Transmitter section. The transmitter circuit, as shown in Fig. 2, is constructed using an encoder IC HT12E (IC2), a 5V voltage