

```

1  const int Pin1 = A0; // First Input pin
2  const int Pin2 = A1; // Second Input pin
3  const int Pin3 = A2; // Third Input pin
4  const int Pin4 = A3; // Forth Input pin
5  const int buzz = 8;
6  int State1 = 0; // variable for reading the First status
7  int State2 = 0; // variable for reading the Second status
8  int State3 = 0; // variable for reading the Third status
9  int State4 = 0; // variable for reading the Forth status
10 #include <LiquidCrystal.h>
11 const int rs = 12, en = 11, d4 = 5, d5 = 4, d6 = 3, d7 = 2;
12 LiquidCrystal lcd(rs, en, d4, d5, d6, d7);
13 void setup() {
14     Serial.begin (9600);
15     pinMode(Pin1, INPUT);
16     pinMode(Pin2, INPUT);
17     pinMode(Pin3, INPUT);
18     pinMode(Pin4, INPUT);
19     pinMode(buzz, OUTPUT);
20     digitalWrite(buzz,LOW);
21     lcd.clear();
22 }
23 void loop() {
24     State1 = digitalRead(Pin1);
25     State2 = digitalRead(Pin2);
26     State3 = digitalRead(Pin3);
27     State4 = digitalRead(Pin4);
28     if (State1 == LOW) {
29         lcd.begin(16, 2);
30         digitalWrite(buzz,HIGH );
31         delay(5000);
32         digitalWrite(buzz,LOW );
33         lcd.print("BREAKFAST");
34         delay(10000);
35         lcd.clear();
36     }
37     else
38     if (State2 == LOW) {
39         lcd.begin(16, 2);
40         digitalWrite(buzz,HIGH );
41         delay(5000);
42         digitalWrite(buzz,LOW );
43         lcd.print("LUNCH");
44         delay(10000);
45         lcd.clear();
46     }

```

Fig. 4: Code snippet

regulator 7805 (IC3), a 433MHz RF transmitter (RF1), four push-to-on switches (S1 through S4), a 1-mega-ohm resistor (R1), and additional components. The transmitter operates without requiring source code.

Receiver section. The receiver circuit, shown in Fig. 3, includes a decoder IC HT12D (IC1), a 5V power supply, a 433MHz RF receiver module (RF2), an Arduino Uno board (MOD1), a 16x2 LCD

(MOD2), four LEDs (D1 through D4), a buzzer (B1), and other components. The receiver section must be programmed to process incoming signals and display the relevant output on the LCD while activating the buzzer. The code is written using the Arduino IDE.

An alternative receiver circuit, which uses an I2C display, is shown in Fig. 4. The prototype for this circuit is not included.

Circuit operation

The 433MHz transmitter and receiver RF modules (RF1, RF2) allow

wireless signal transmission. The system operates by interfacing the Arduino Uno, the 433MHz transmitter and receiver modules, and the LCD. When a switch is pressed (or, with the glove, when a finger touches the thumb), the transmitter sends a signal wirelessly. This signal is received by the 433MHz receiver (RF2), which is indicated by a brief blink from the blue LED. The signal is also routed to the analogue input pins of the Arduino Uno.



Don't Be A Loser!

You don't know how much you don't know.

Read

electronics FOR YOU

to keep up-to-date with the tech world



To subscribe, visit efy.in or contact us at: 011-4059660
Email: support@efy.in

OR

Scan This Code



Also available at all leading magazine outlets