

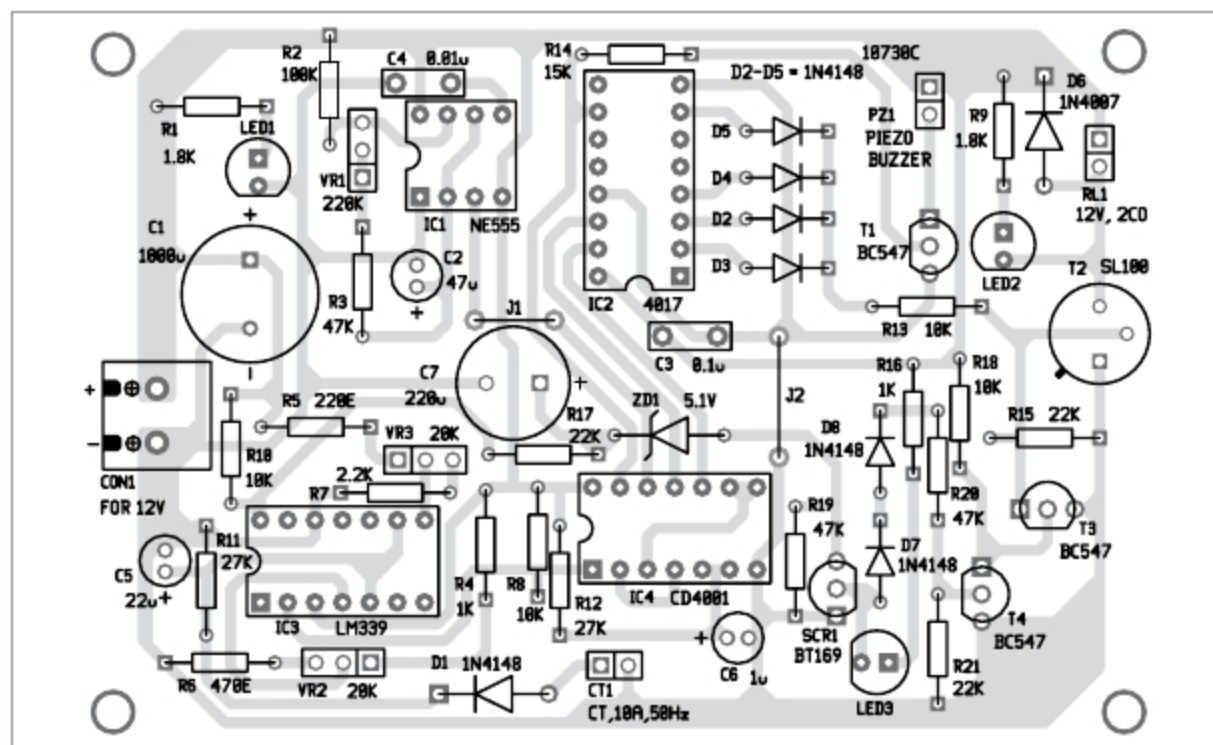


Fig. 4: Components layout for the PCB

alignments, measure sample voltage from the rectifier at cathode of D1 using a digital multimeter. A window of sample voltage for safe operation of an electrical circuit must be decided with an upper limit and lower limit. Adjust VR2 to lower limit voltage across its variable arm and ground,

and adjust VR3 to upper limit voltage across its variable arm and ground.

For example, if the rectifier is providing a DC sample voltage of 6V on normal-load condition, you can decide the window between 5V and 8V. (Since sufficient delay is provided for no-load condition, any instantane-

ous or brief no-load conditions will not affect the normal operation of the circuit.) Set the voltage across variable arm of VR2 and ground to 5V, and voltage across variable arm of VR3 and ground to 8V.

Current transformer. Basic primary current is 1A, and maximum primary current is 10A. Operating frequency is 50Hz, while winding ratio is 1:1200.

Notes. 1. Only live (phase) wire of load side should be passed through the current transformer (CT1).

2. You can use 12V, 1A SMPS in place of 12V DC power supply.

3. Input AC supply to 12V SMPS should be taken after switch S1 powers on, so that entire circuit resets by switching off and on S1 after an alarm condition arises. **EFY**



Santhosh.C.C is working as assistant general manager in Airports Authority of India, Bengaluru. He has an experience of more than 28 years in the maintenance of electronics equipment

Leaded Passive Components Think Thakor

THAKOR ELECTRONICS LIMITED



Metal Glazed Resistors (MGR)

Provide high stable performance against environmental conditions & overload voltages.



Wire Wound Resistors (WWR)

Small dimension, excellent stability in high temperature, resistant to humidity and comparatively than other kind of resistor. Fabricated using a suitable fiberglass or ceramic core with resistance wire securely crimped to the terminals. Precise resistance value with better life proof. Super heat dissipation, small linear temperature coefficient. Instant over load capability, low noise figure and without annual shift on resistance value.

Some of our segments we actively deal


1. Automobile
2. Lighting
3. Power Industry
4. Electrical Industry
5. Instrumentation
6. Consumer Industry & Others

Manufacturers of

- CFR • MFR • MOR • MGR
- WWR • Fusible Resistors
- High Power Resistors
- Aluminium Housed Breaking Resistors



Gold-Aluminum-Housed-Resistor

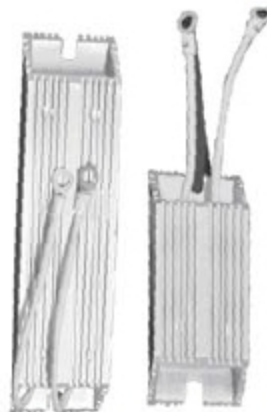

Aluminum-Housed-Resistor Breaking Resistor



Precision-High-Voltage-Resistor

Email: mktg@thakorelectronics.com Tel: (02522)280277, 08390290835

www.thakorelectronics.com