

Low-Cost Versatile HAND MIXER

PRANAV R. ROKDE AND SHUBHAM P. TALKHANDE

Mixing liquids using a muddler or churner is a traditional technique. However, it is time consuming and sometimes fails to mix these properly. Here is a low-cost and versatile hand mixer circuit. It can be used for making stuff like

lassi, chhach (buttermilk), butter and lemonade, among others. The author's prototype is shown in Fig. 1.

Circuit and working

The circuit diagram of the low-cost and versatile hand mixer is shown in Fig.

2. It is built around 5V voltage regulator 7805 (IC1), two BC547 transistors (T1 and T2), motor driver L293D (IC2), 12V geared motor (M1) and a few other components.

Transistors T1 and T2 along with resistors R2 through R5 and capacitors C2 and C3 are configured as an astable

multivibrator. Resistors R2 and R5 are connected as pull-up resistors. Resistors R3 and R4, and C2 and C3 are used for time period constants. You may change these values as per your requirement.

IC2 is used to drive motor M1. It is a dual H-bridge motor driver IC for driving the motor in clockwise as well as anti-clockwise directions.

IC1 (7805) is used as a power supply regulator. It gives constant 5V supply to power the astable multivibrator and IC2. Resistor R1 connected with LED1 is used to indicate power-on status. You can power up the circuit by connecting the power supply to connector CON1 using either 12V battery, 12V adaptor or 12V solar panel.

The churner is built around a DC geared motor. Its working is the same



Fig. 1: Author's prototype



Fig. 3: A typical churner

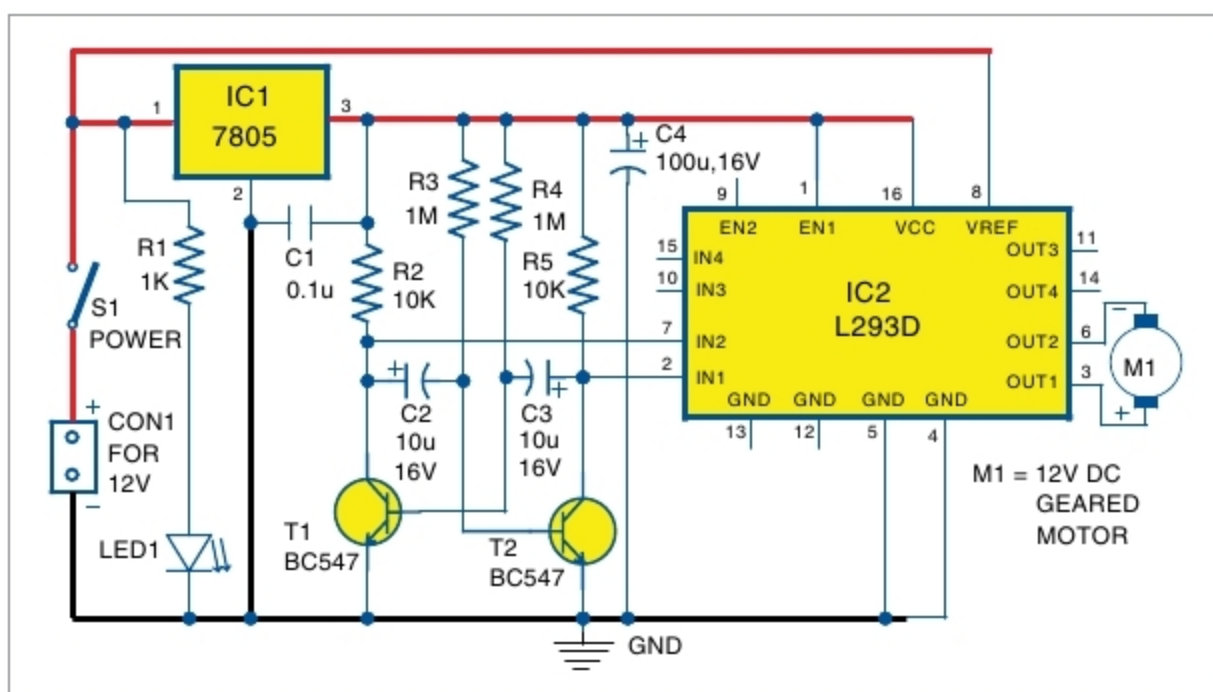


Fig. 2: Circuit diagram of low-cost and versatile hand mixer

PARTS LIST

Semiconductors:

- IC1 - 7805, 5V voltage regulator
- IC2 - L293D motor driver
- T1, T2 - BC547 npn transistor
- LED1 - 5mm LED

Resistors (all 1/4-watt, $\pm 5\%$ carbon):

- R1 - 1-kilo-ohm
- R2, R5 - 10-kilo-ohm
- R3, R4 - 1-mega-ohm

Capacitors:

- C1 - 0.1 μ F ceramic disk
- C2, C3 - 10 μ F, 16V electrolytic
- C4 - 100 μ F, 16V electrolytic

Miscellaneous:

- S1 - On/off switch
- CON1 - 2-pin terminal connector
- M1 - 12V, 500- to 1000-rpm geared motor
- 12V battery/adaptor
- Muddler/churner

THE COMPLETE MAGAZINE ON OPEN SOURCE

OpenSource
ForYou

The latest from the Open Source world is here.

OpenSourceForU.com

Join the community at facebook.com/opensourceforu

Follow us on Twitter @OpenSourceForU