

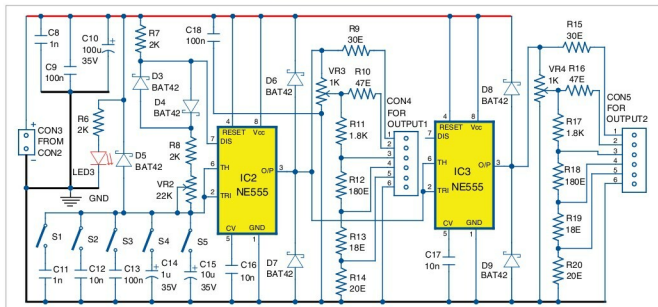


Fig. 2: Circuit diagram of signal generator

through D9 protect timer outputs from over-voltage and under-voltage.

Construction and testing

An actual-size PCB layout for the power supply is shown in Fig. 3 and

its components layout in Fig. 4. After assembling the circuit on the PCB, connect the line (L) and neutral (N) to 230V AC mains supply. Variable power supply for the signal generator section is available at CON2. Connect

LED1 and LED2 on the front panel for power-status indications. The circuit can be powered by either 230V AC, 50Hz mains power supply with transformer X1 or 15V DC power supply connected to CON1.



Would You Like More DIY Circuits?

We Have Thousands!

VISIT TODAY

electronicsforu.com

If it's electronics, it's here