



AC LAMP BLINKER

Using Timer NE555

PETRE TZV PETROV

There are at least two popular applications of blinking a string of 110V/230V AC incandescent lamps. The first is audio-visual warning at construction sites or where repairing is going on. The second is to express joy and excitement during holidays like New Year's Day.

Here we use a very simple and low-cost timer NE555 to switch on and off two output loads alternately for audio and visual indications. You can achieve this by using a bipolar-transistor-based NE555 or CMOS-based LMC555.

This circuit can be made to blink

AC lamps at a low frequency, or switch on and off electrical loads connected to the mains at a low speed. In order to reduce the RF emissions, switching is done only at zero crossings of the mains AC voltage.

The switching frequency is selected according to the resistor and capacitor components connected to NE555. It can be varied using 100-kilo-ohm potmeter VR1.

Circuit and working

Circuit diagram of the AC lamp blinker is shown in Fig. 1. It is built around a step-down transformer (X1), 9V voltage regulator 7809 (IC1), timer NE555 (IC2), two MOC3043 optoisolators (IC3 and IC4), two BT406 triacs (Triac1 and Triac2), two 1N4007 diodes (D1 and D2), six LEDs (LED1 through LED6), two piezo-buzzers (PZ1, PZ2), two 230V AC, 60W bulbs (Load1 and Load2), and a few other components.

PARTS LIST

Semiconductors:

- IC1 - 7809, 9V regulator
- IC2 - NE555 timer
- IC3, IC4 - MOC3043 optoisolator
- D1, D2 - 1N4007 rectifier diode
- BR1 - 1A bridge rectifier
- Triac1, Triac2 - BT406 triac
- LED1-LED6 - 5mm LED

Resistors (all 1/4-watt, $\pm 5\%$ carbon, unless stated otherwise):

- R1 - 100-ohm, 1-watt
- R2 - 1-kilo-ohm
- R3, R5 - 10-kilo-ohm
- R4 - 33-kilo-ohm
- R6-R8 - 330-ohm
- R9, R10, R12, R15 - 220-ohm
- R11, R13, R16 - 100-kilo-ohm
- R14, R17 - 100-ohm, 0.5-watt
- VR1 - 100-kilo-ohm potmeter

Capacitors:

- C1, C8-C11 - 0.1 μ F, 400V polyester
- C2, C5 - 0.1 μ F ceramic disk
- C3 - 470 μ F, 25V electrolytic
- C4, C6 - 100 μ F, 16V electrolytic
- C7 - 0.01 μ F ceramic disk

Miscellaneous:

- CON1-CON3 - 2-pin terminal connector
- F1 - 0.1A fuse with holder
- F2, F3 - 1A fuse with holder
- PZ1, PZ2 - Piezo-buzzer
- SI-S4 - On/off switch
- Load1, Load2 - 230V AC, 60W bulb/lamp
- X1 - 230V AC primary to 12V, 250mA secondary transformer
- 230V AC mains power supply
- Heat-sinks for triacs
- Mains power cord

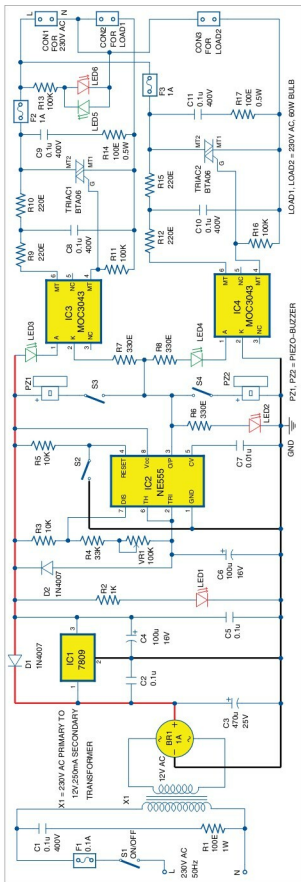


Fig. 1: Circuit diagram of AC lamp blinker using timer NE555