

Dual AUDIO LEVEL SHIFTER And BUFFER For ADCs, MCU Kits And Arduino

PETRE TZV PETROV

Many single-ended analogue signals do not have DC components or appropriate DC offsets. Due to that, these require very high input resistance for analogue-to-digital converter (ADC) inputs. This simple universal dual level shifter and buffer for AC and audio signals can be used for ADCs, MCU kits and Arduino. It does not need any special adjustment to work properly. Before using the circuit, select and adjust the appropriate DC offset for each operational amplifier, every time.

We need analogue level shifters and buffers between the source of analogue signals (AC or audio) and inputs of the ADC. Here, we see a simple solution for two channels of the ADC. The circuit can be multiplied for any number of ADC inputs.

Circuit and working

Circuit diagram of the dual and audio level shifter and buffer for ADCs, MCU kits and Arduino is shown in Fig. 1.

The circuit has two analogue channels. In each channel, there is a single operational amplifier working as a level shifter and buffer follower. Input AC or audio signal is applied to input1 and input2. Input resistance at low frequency is around 1-mega-ohm. Bandwidth of each channel is 2Hz to more than 100kHz.

SELECTION OF DC OFFSETS

Closed jumper	Function
SJ1	Offset $V_{cc}/2$ for A1 of IC1, here $V_{cc}=5V$
SJ2	Offset $V_{cc}/2$ for A2 of IC1, here $V_{cc}=5V$
SJ3	Adjustable DC offset with VR1 for A1 of IC1
SJ4	Adjustable DC offset with VR2 for A2 of IC1

PARTS LIST

Semiconductors:

- IC1 - MCP602 op-amp
- D1 - 1N4007 rectifier diode
- D2-D8 - 1N4148 signal diode
- LED1 - 5mm LED

Resistors (all 1/4-watt, $\pm 5\%$ carbon):

- R1, R4 - 300-ohm
- R2, R3, R8, R9, R11 - 1-kilo-ohm
- R5, R12 - 1-mega-ohm
- R6, R10 - 100-ohm
- R7, R13 - 100-kilo-ohm
- VR1, VR2 - 10-kilo-ohm potentiometer

Capacitors:

- C1 - 220 μ F, 16V electrolytic
- C2-C4 - 100nF ceramic disk
- C5-C7 - 100 μ F, 16V electrolytic

Miscellaneous:

- CON1 - USB type A connector
- CON2, CON3 - 2-pin connector
- CON4-CON7 - 2-pin berg strip
- CON8, CON9 - 2-pin terminal connector
- F1 - 100mA fuse with holder
- SJ1-SJ4 - Shorting jumper

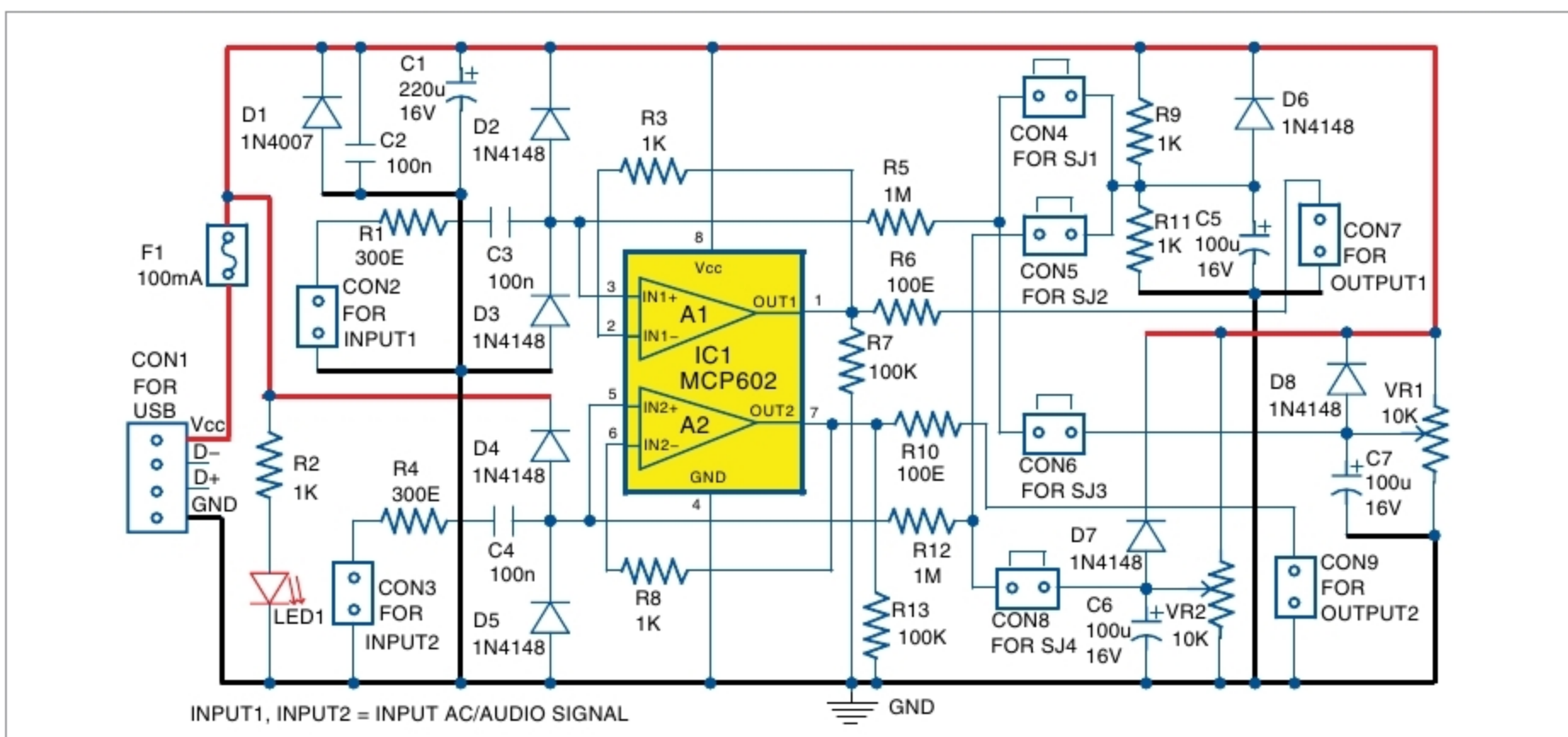


Fig. 1: Circuit diagram of dual level shifter and buffer