

and T2, transformer X1, bridge rectifier BR1 and voltage regulator 7808 (IC5). The output of IC1 is fed to relay

RL1 through the inverter built around transistors T1 and T2. If battery voltage goes above 5.5V, the circuit

PARTS LIST

Semiconductors:

- IC1-IC4, IC6 - 741 operation amplifier
- IC5 - 7808, 8V voltage regulator
- T1-T3 - 2N2222 npn transistor
- LED1-LED6 - 5mm LED
- D1-D3 - 1N4007 rectifier diode
- BR1 - 1A, bridge rectifier

Resistors (all 1/4-watt, $\pm 5\%$ carbon):

- R1 - 4.7-kilo-ohm
- R2, R3, R5-R7, R9, R16 - 1-kilo-ohm
- R4, R8, R10, R11, R14, R15 - 560-ohm
- R12 - 2-kilo-ohm
- R13 - 470-ohm
- VR1, VR2 - 1-mega-ohm potentiometer
- LDR1 - LDR

Capacitors:

- C1 - 470 μ F, 25V electrolytic
- C2 - 0.1 μ F ceramic disk

Miscellaneous:

- BATT.1 - 6V rechargeable battery
- CON1 - 3-pin connector
- CON2, CON3 - 2-pin terminal connector
- S1, S2 - SPDT switch
- RL1, RL2 - 12V single-changeover relay
- X1 - 230V AC primary to 12V, 1A secondary transformer
- PS - ± 12 V power supply (PS) with 2-pin terminal connector

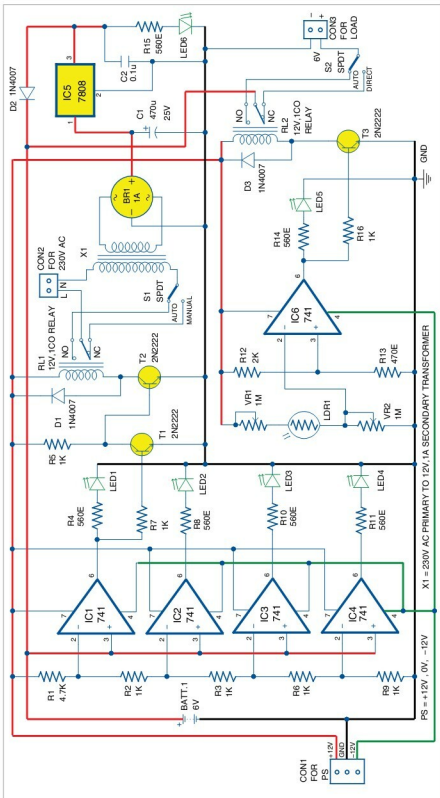


Fig. 2: Circuit for automatic light and overcharging control

de-energises relay RL1 to prevent overcharging. If voltage level is less than 5.5V, it energises RL1 to start battery charging.

Switch S1 is used to charge the battery in either manual or auto mode. In manual mode, it provides direct path to charge the battery. But this mode has a drawback: When you forget to switch off S1, the battery will get overcharged. In auto mode, the battery is charged on-load or off-load with overcharging protection. Table 1 shows LED indication and relay status for different battery voltage levels.

Diode D2 provides unidirectional signal flow for battery charging from 8V DC supply.

Automatic light control. This unit is built around IC6, light-dependent resistor LDR1, transistor T3 and relay RL2. LDR1 provides control voltage to comparator IC6. You can control the sensitivity of LDR1 using potentiometers VR1 and VR2. As per the setting of light intensity in LDR1, relay RL2 energises through T3 to switch on the load.

Switch S2 is used to activate the load in either direct or auto mode.