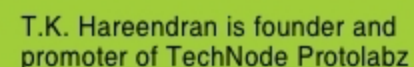




The circuit safely charges the battery up to 4.20V through T2 and IC2, together with charge current-limiter resistors R1 and R2. LED1 lights up when charging current is $>120\text{mA}$, while LED2 glows to indicate charger/battery status. Usually, LED2 lights up

For the enclosure, use a small acrylic homemade box, or a 3D-printed one. Once the board is populated and tested, put the circuit (with battery) in the enclosure. The author used a translucent biscuit tin as an enclosure (Fig. 5). **EFY**



If it's electronics, it's here