

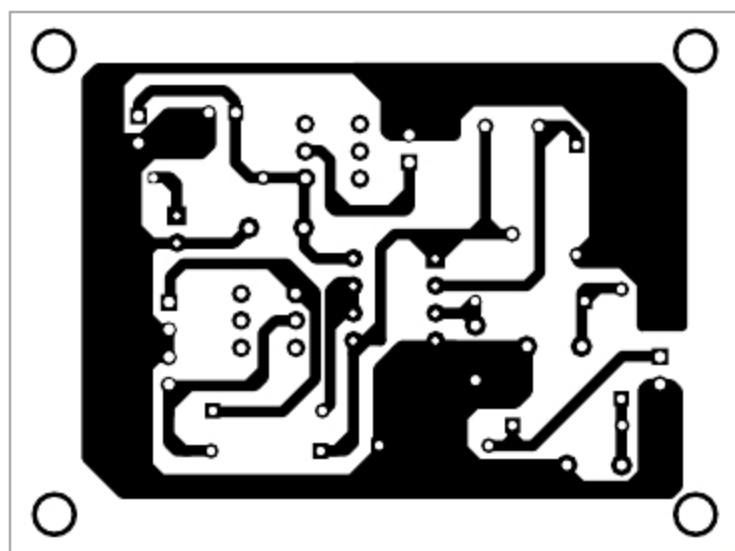


Fig. 3: Actual-size PCB layout of PWM-to-analogue signal converter

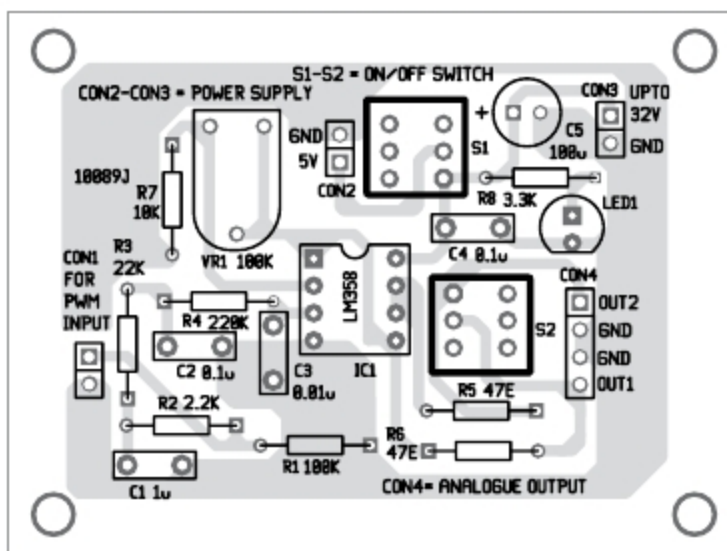


Fig. 4: Components layout for the PCB

EXAMPLES OF REFERENCE VOLTAGES FOR TESTING THE CIRCUIT

Square-wave signal T_{ON}/T_i (%)	Approximate V_{out} as percentage of $V_{out_{max}}$	Example of V_{out} , if $V_{out_{max}} = 5.000V$ needed	Example of V_{out} , if $V_{out_{max}} = 3.000V$ needed
0	0	$0.0V = V_{out_{min}}$	$0.0V = V_{out_{min}}$
10	10	0.5V	0.3V
20	20	1V	0.6V
30	30	1.5V	0.9V
40	40	2.0V	1.2V
50	50	2.5V	1.5V
60	60	3.0V	1.8V
70	70	3.5V	2.1V
80	80	4.0V	2.4V
90	90	4.5V	2.7V
100	100	$5.0V = V_{out_{max}}$	$3.0V = V_{out_{max}}$

OA2 works as a follower, where gain $A_{v2} = +1$

Construction and testing

An actual-size PCB layout of the PWM-to-analogue converter is shown in Fig. 3 and its components layout in Fig. 4.

Before testing, note that, maximum output voltages (V_{out}) at OUT1

and OUT2 depend on: power supply of operational amplifiers, position of potentiometer VR1 and output voltage levels of TTL/CMOS output driving the module.

To test the circuit, fix the frequency of PWM (for example, 1000Hz) and change the duty cycle time period T_{ON} and T_{OFF} of the pulses. Refer to the table to test output voltages.

PARTS LIST

Semiconductors:

- IC1 - LM358, op-amp
- LED1 - 5mm LED

Resistors (all 1/4-watt, $\pm 5\%$ carbon):

- R1 - 100-kilo-ohm
- R2 - 2.2-kilo-ohm
- R3 - 22-kilo-ohm
- R4 - 220-kilo-ohm
- R5-R6 - 47-ohm
- R7 - 10-kilo-ohm
- R8 - 3.3-kilo-ohm
- VR1 - 100-kilo-ohm preset

Capacitors:

- C1 - 1 μ F, ceramic disc
- C2, C4 - 0.1 μ F, ceramic disc
- C3 - 0.01 μ F, ceramic disc
- C5 - 100 μ F, 50V electrolytic

Miscellaneous:

- CON1-CON3 - 2-pin connector
- CON4 - 4-pin connector
- S1-S2 - On/off switch
- 5V DC power supply

Linearity of the conversion depends, to some degree, on the parameters of the digital output. A too low or too high PWM duty cycle should be avoided. Usually, duty cycle of PWM $< 5\%$ and $> 95\%$ must be avoided. In most cases, PWM DACs are good for driving LEDs, incandescent lamps, LCD displays, DC motors and loudspeakers, among others.

Spectrum of the rectangular signal produced by the PWM is large and variable. This can be a problem without appropriate filtering, construction and PCB layout. Resistors, capacitors and operational amplifiers for filtering and buffering of PWM signals should have appropriate characteristics. Usually with PWM

DACs, you obtain high resolutions but not accuracy. **EFY**



Petre Tzv Petrov was a researcher and assistant professor in Technical University of Sofia (Bulgaria) and expert-lecturer in OFPPT(Casablanca), Kingdom of Morocco. Now, he is working as an electronics engineer in the private sector in Bulgaria

THE COMPLETE MAGAZINE ON OPEN SOURCE

OpenSource
ForYou

The latest from the Open Source world is here.

OpenSourceForU.com

Join the community at facebook.com/opensourceforu

Follow us on Twitter @OpenSourceForU