

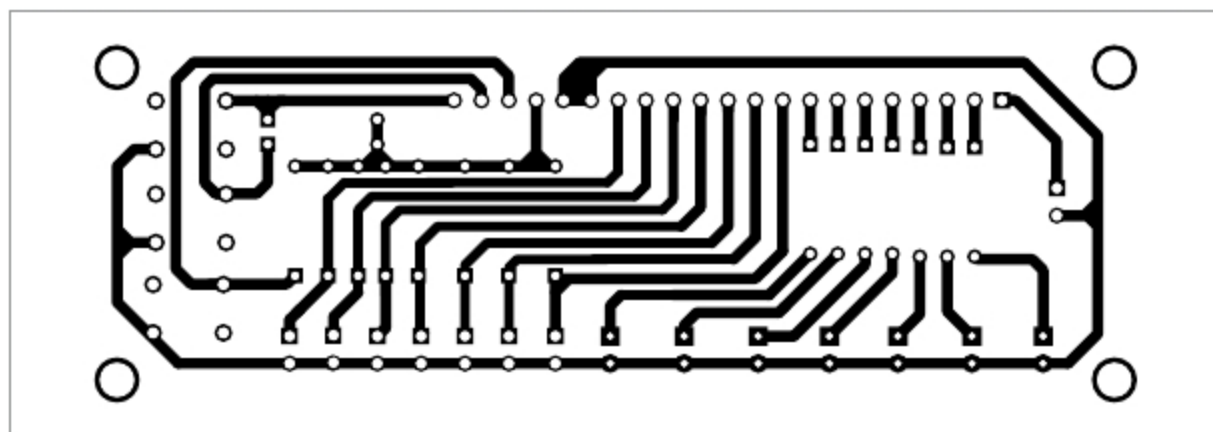


Fig. 3: Actual-size PCB layout of the window alarm annunciator

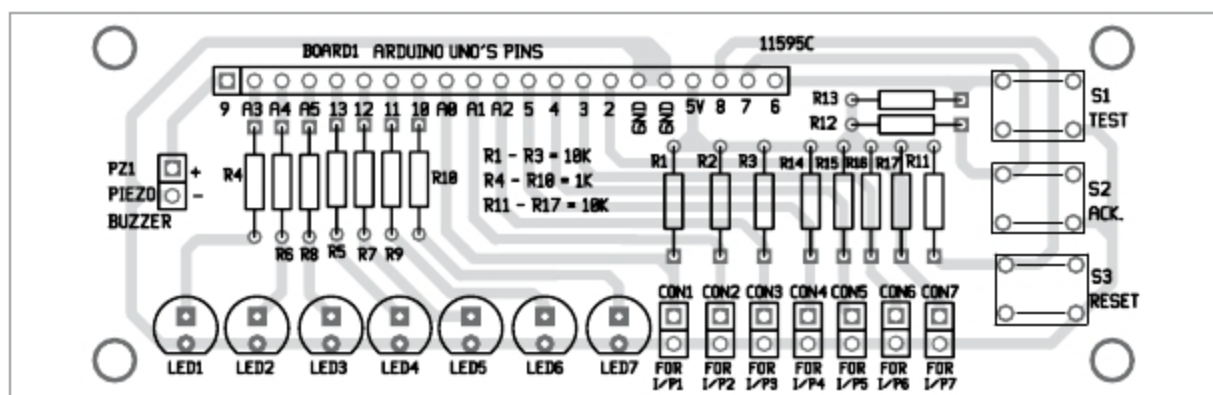


Fig. 4: Components layout for the PCB

PARTS LIST

Semiconductors:

Board1 - Arduino Uno board
LED1-LED7 - 5mm LED

Resistors (all 1/4-watt, $\pm 5\%$ carbon):

R1-R3, R11-R17 - 10-kilo-ohm
R4-R10 - 1-kilo-ohm

Miscellaneous:

S1-S3 - Tactile switch
CON1-CON7 - 2-pin connector
- Arduino Uno board with boot loader
- Jumpers
- 21-pin male Berg strip connector

by following the steps given below.

Sketch > Include libraries > Add. ZIP Library... > and browse the location where elapsedMillis file is saved. After adding the above library function, ensure that it appears in the list of library functions. Now, upload Annunciator.ino sketch file to the board.

Construction and testing

An actual-size PCB layout of the window alarm annunciator is shown in Fig. 3 and its components layout in Fig. 4. After assembling the circuit, enclose it in a suitable box, along with Arduino Uno. Fix all LEDs on one side

of the cabinet and piezo buzzer on the other. Power supply for the circuit is used through Arduino board and connected through the USB port of the laptop/desktop.

All inputs, I/P1 through I/P7, are potential-free external NO contacts with a common ground rail. That is, all inputs coming from the appliances/machineries should be NO. Input contacts should close when problems like overload or short-circuit occur in the load of one or more appliances/machineries.

For easy and quick testing, assemble the circuit on a breadboard, as per the given connection diagram. All inputs can be initiated, including acknowledge, test and reset inputs, by pressing the respective switches.

Caution. 1. Only potential-free external NO contacts should be used as alarm contacts (CON1 through CON7) with a common ground. Otherwise, external voltage injected into the circuit will damage Arduino Uno.

2. If long cables are used for alarm input, EMI suppression circuits/optocoupler circuits should be added to prevent spurious operation or damage. **EFY**



P. Balasubramanian is a retired scientific officer from Nuclear Power Corp. of India Ltd (NPCIL). His areas of interest include microcontrollers and power electronics

EFY Note

The source code of this project is available for free download at source.efymag.com

Share Your Knowledge

If you are an expert in your field of electronics, why not share your knowledge with the world?



Electronics For You invites electronics professionals and industry experts to write articles on their area of expertise and interest from different perspectives

Some of the topics we want you to write about are:

- Smart World
- Artificial Intelligence
- Autonomous Cars
- Bio-Medical (Healthcare)
- Strategic (Defence) Electronics
- Audio-Video
- Project Reports

So if you have an interesting topic or original article to share, please let us know at efyeditorial@efyindia.com

We would love to hear your good ideas too!

electronics
FOR YOU