

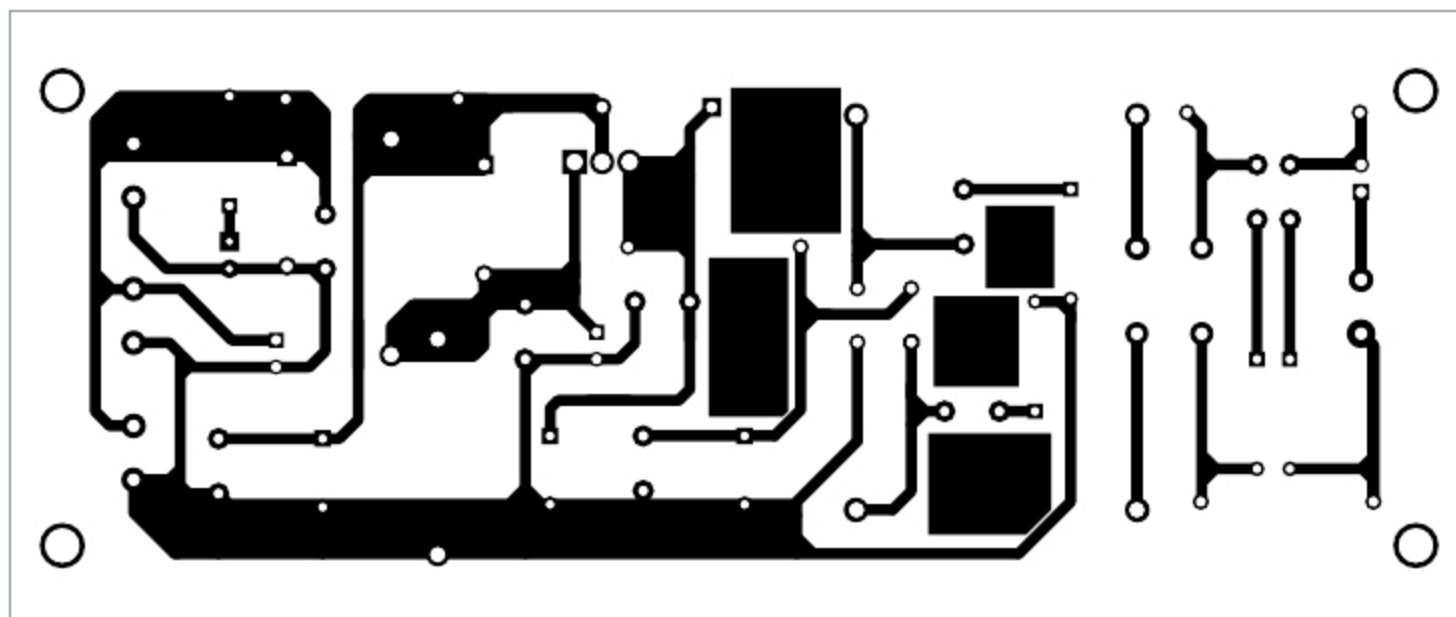


Fig. 2: Actual-size PCB layout of the 48V regulated power supply

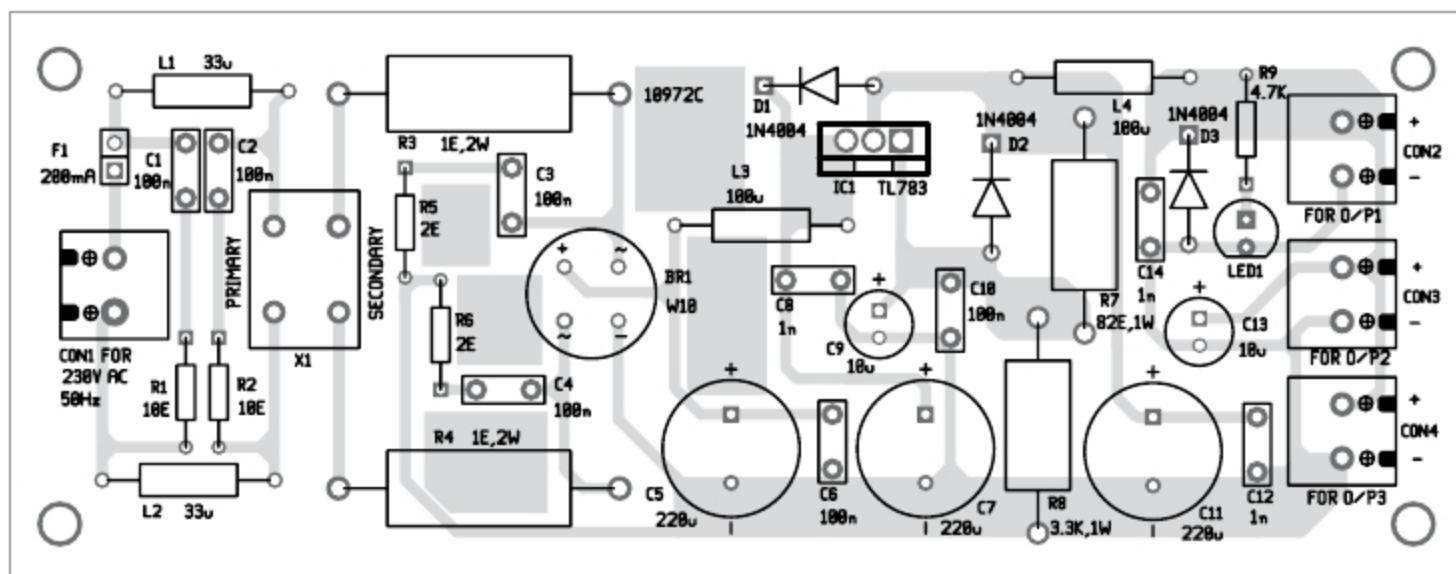


Fig. 3: Components layout for the PCB

reduce the noise from IC1. Diodes D1, D2 and D3 protect IC1. Resistors R7 and R8 fix output regulated voltage V_{out} . Inductor L4 and capacitors C13 and C14 further filter output voltage from IC1.

The circuit has three outputs (O/P1 through O/P3), with 48V phantom power supply from each to drive up to three different circuit applications. LED1 shows the presence of output voltage.



Petre Tzv Petrov was a researcher and assistant professor in Technical University of Sofia (Bulgaria) and expert-lecturer in OFPPT(Casablanca), Kingdom of Morocco. Now he is working as an electronics engineer in the private sector in Bulgaria

Construction and testing

An actual-size PCB layout for the 48V regulated power supply is shown in Fig. 2 and its components layout in Fig. 3. After assembling the circuit on the PCB, enclose it in a suitable cabinet.

Fix transformer X1 on the body of the cabinet, and connect its primary and secondary on the PCB. Also, connect 230V AC mains across CON1. Fix LED1 on the front panel, and CON2 through CON4 on the rear side for the output loads.

The circuit does not need any adjustment to operate properly. **EFY**

To read more stories about electronics manufacturing

ELECTRONICS
ELECTRONICS B2B INDUSTRY
AT THE CLICK OF A BUTTON

Log on to

electronicsb2b.com

www.electronicb2b.com

Log on to www.electronicb2b.com and be in touch with the electronics B2B fraternity 24x7