

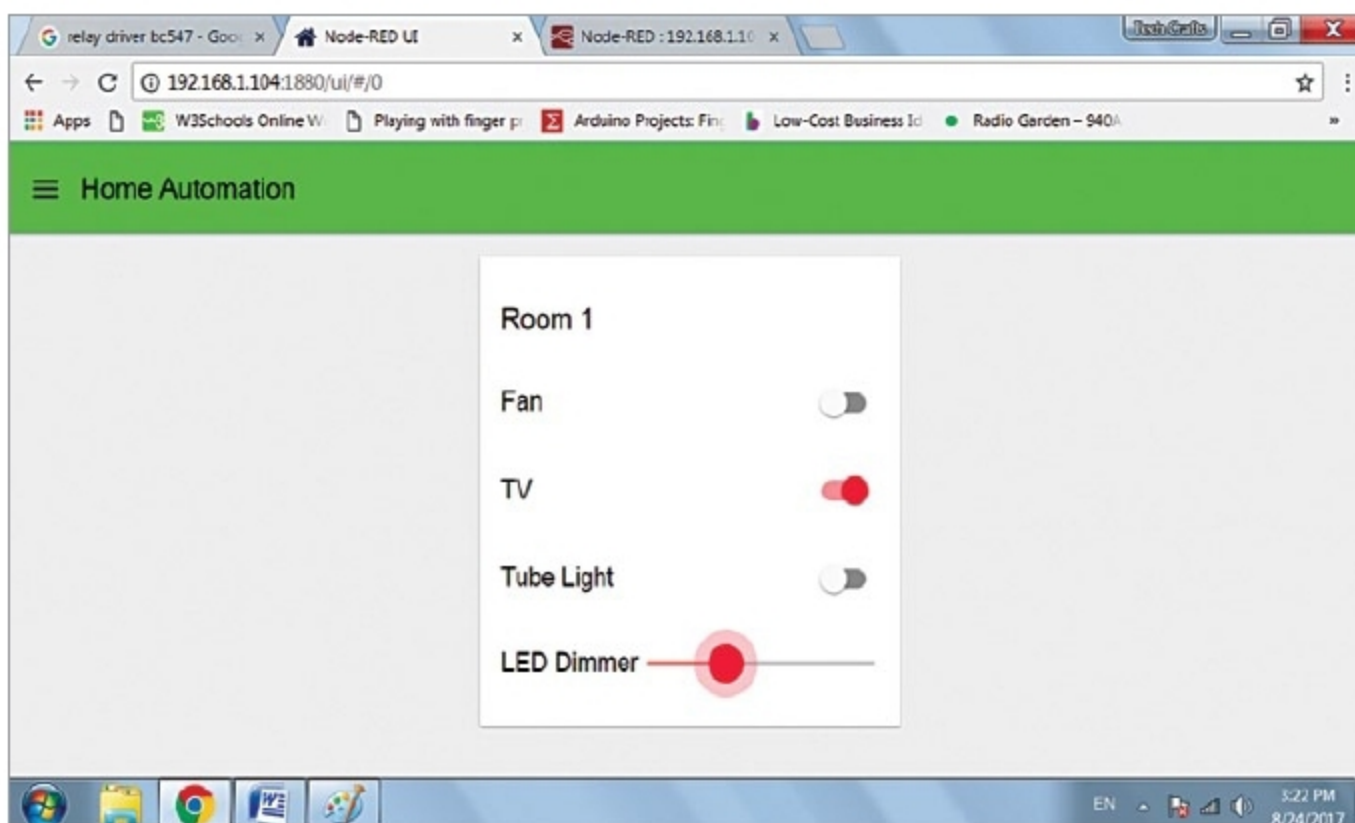


Fig. 12: Final UI of Node-RED

The final UI screen will appear as shown in Fig. 12. You will see three slide switches and a slider. Using the switches, you can turn on or turn off the loads. The slider is used to control

the light intensity of the LED connected to GPIO pin of Raspberry Pi.

When you operate the switch on the UI, corresponding GPIO pin of Raspberry Pi becomes high. Logic

high signal at the base of the transistor makes it to conduct, current flows through it and the corresponding relay is energised. This turns on the corresponding electrical load.

GPIO pin of Raspberry Pi connected with transistor T4 is configured as PWM output. Slider in Node-RED UI makes the variation in PWM pulses. Pulses are fed to the base of T4 that drives a white LED. Pull the slider up and down using a mouse. You will see variations in PWM signal at its base, and light intensity of the LED will vary, accordingly. **EFY**



Jayvardhan Pandit is working as an IoT-based product developer and PCB designer at Germanium Instruments Pvt Ltd, Bhopal

www.powerasia.in



POWER Asia
Energising Power Industry

10, 11 & 12 Aug. 2019, Pragati Maidan, New Delhi

Specialised Exhibition on Power Technology

⦿ VOLTAGE STABILIZERS	⦿ BATTERIES
⦿ UPS SYSTEMS	⦿ SWITCHGEARS
⦿ TRANSFORMERS	⦿ CONTROL PANELS
⦿ INVERTORS	⦿ WINDING WIRES
⦿ GENERATORS	⦿ L.E.D. LIGHTS

SOLAR PRODUCTS, POWER TOOLS,
COMPONENTS AND
ALLIED INDUSTRIES

Prime Sponsor



Main Sponsor



Associate Sponsor



Media Partner



Approved by



Organised by : CREATIVE EDGE T: +91-11-42471061, 42471063 M: +91-9811707020 E : powerasia19@gmail.com, prkmedia@gmail.com