

TABLE I
THICKNESS OF VARIOUS
BUTTON CELLS

Battery IEC names	Dimensions in mm (Diameter×Height)
CR2016	20×1.6
CR2020	20×2
CR2025	20×2.5
CR2032	20×3.2

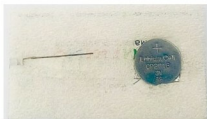


Fig. 7: Placing LED and battery on the foam

tape with aluminium foil. Take a sheet of aluminium foil and give it several folds because most aluminium foils are too thin to use. The



Fig. 8: Placing the other card over the foam



Fig. 9: Final assembly of the business card flashlight

aluminium tape formed by folding aluminium foil is shown in Fig. 5.

Step 4. Assembling the circuit. Pull the LED legs apart and place one leg along the pencil trace and stick on the card with the aluminium tape using adhesive (Fig. 6).

Note the correct polarity of the LED leads so as to place the battery correctly. Aluminium tape should extend till the battery (Fig. 6). Place the foam cutout over it and stick on the card using adhesive (Fig. 7).

Step 5. Final step. Carefully place the second card over the LED and battery so that the hanging leg of the LED is fixed onto the backside of the second card using aluminium tape (Fig. 8). Place it in a secure manner using adhesive like Fevicol.

Press the switch marked on the card. Voila, it is up and running (Fig. 9)! When you release the switch, flashing will stop. You have successfully made one unique business card with a flashlight! **EFY**



Prem Sagar is founder and chief executive officer, Banaao—A Maker's Playground



Would You Like More DIY Circuits?

We Have Thousands!

VISIT TODAY

electronicsforu.com

If it's electronics, it's here