

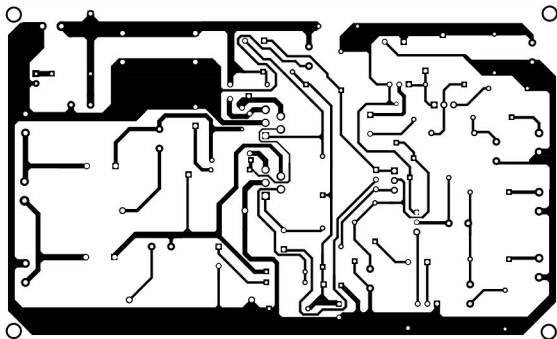


Fig. 2: Actual-size PCB layout of the simple dual-way amplifier for one microphone and two guitars

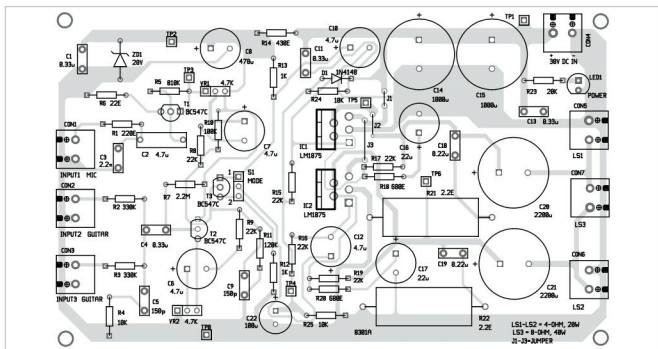


Fig. 3: Component layout of the PCB

Theoretically, if two power amplifiers are bridged, the output power increases four times. Practically, there are limitations imposed by the parameters of the ICs. More information about bridging is provided in the datasheets of respective ICs.

Selection of ICs from Table I will determine the minimum and maximum power supply, minimum output load resistance, maximum output and maximum power dissipation of the semiconductors.

Connectors. The amplifier has

seven connectors (CON1-CON7). There are three inputs (CON1-CON3), three outputs (CON5-CON7). CON4 is for power supply. Input signal from a microphone is applied to CON1 and is amplified through T1. Gain of the stage is