

Sound-Operated TIMER

PRADEEP G.

This sound-operated timer is based on LM324 quad-operational amplifier and NE555

multivibrator. Sound signal, like clapping, sensed by condenser microphone MIC1 is amplified by IC1.

Amplified signal is fed to trigger pin 2 of IC2. Output pin 3 of IC2 goes high and relay RL1 gets ener-

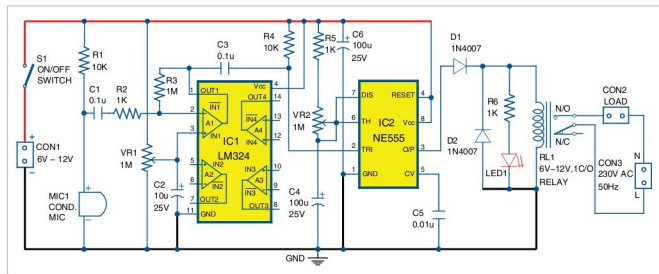


Fig. 1: Circuit diagram of the sound-operated timer

timer. Time delay can be set from a few seconds to 30 minutes. It can also be used as a sound-sensitive burglar alarm.

Circuit and working

Circuit diagram of the sound-operated timer is shown in Fig. 1. Output pin 1 of LM324 (IC1) is fed to pin 2 of NE555 (IC2) through capacitor C3. IC2 is configured as a monostable

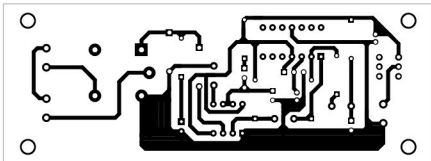


Fig. 2: Solder-side PCB layout of the sound-operated timer

THE COMPLETE MAGAZINE ON OPEN SOURCE

OpenSource
ForYou

Your favourite Magazine on
Open Source is now on the Web, too.

OpenSourceForU.com

Follow us on Twitter@LinuxForYou