



FEEDBACK

YOUR SUGGESTIONS

3-PHASE INDUCTION MOTOR

In 'Controlling 3-Phase Induction Motors Using VFD and PLC' article published in April issue, I tried to control the speed of a stepper motor with Omron PLC and VFD but in vain. Please help.

Muhammad Saleem Ullah
Through email


The author Joby Antony replies:
The article talked about how 3-phase induction motors can be controlled using VFD and PLC. Stepper motors work altogether differently as these are pulse-driven, whereas induction motors are AC-driven. Therefore this project cannot be used directly for stepper motor control. However, since any PLC uses relays, one must connect each coil of the stepper motor through a relay for controlling it.

12V BATTERY CHARGER

I liked the '12V Battery Charger Cum Variable Power Supply' DIY article published in November 2016 very much. Kindly add a voltmeter and ampere meter to the circuit. It would be of great help.

Patrick Vaz
Through email

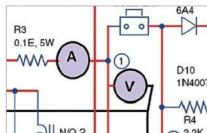The author Fayaz Hassan replies:
Voltmeter can be connected across point 1 and ground, and ammeter



Circuit of 12V battery charger with voltmeter and ammeter

From electronicsforu.com

Electronics Projects

Can we use Arduino Uno in 'Voice Controlled Home Automation System' project published in October 2016 issue?

Akshay

EFY. Yes, you can use Arduino Uno but make sure you connect R1 to digital pin 6 of Arduino Uno, and pins TXD and RXD of HC-05 to RX0 and TX0 pins of Arduino Uno, respectively.

The '0-50V Variable Power Supply Using LM317' DIY project published in October 2016 issue is really very good.

Ronaldo

EFY. Thanks for the feedback!

can be connected between point 1 and resistor R3. The modified circuit is shown here in the figure with the position of voltmeter marked as V and ammeter as A.

SOUND-OPERATED TIMER

I assembled 'Sound-Operated Timer' DIY project published in January issue. When I clap in front of the mic, it gives output at pin 3 of NE555 (IC2), which doesn't switch to another state as per the time delay set by timing components (VR2 and C4). Output remains on until the supply is turned off. I tried varying VR2 but nothing happens. Please help.

Kunal Khosla
Through email

EFY. First check potmeter VR2 and capacitor C4 for proper connections in the circuit. You may also try replacing capacitor C4 with any one of the values between 1µF and 10µF. Then observe the output after clapping in front of the mic. If you are using 6V at CON1, relay RL1 rating should be 6V.

Otherwise, the circuit will not work properly. You can also test the circuit by removing the relay section including diode D1. Then put a voltmeter across pin 3 of IC2. Check the output voltage before clapping and after clapping. See if the output goes off after a time delay.

LED AS SENSOR

In 'LED as Light Sensor' DIY article published in December 2016 issue, the role of capacitor C1 is not clear. When I removed C1 from the circuit, the output remained the same.

Pragya Rai
Through email

EFY. Here, capacitor C1 acts as an energy storage device. With capacitor C1, white LED2 will glow for some time even when the input is withdrawn. Whenever pin 6 of IC1 goes high, it starts charging and, at the same time, white LED2 glows. When pin 6 goes low, C1 starts discharging. White LED2 glows until C1 discharges completely. The circuit will work without C1 but that is not the main goal of the design.

MICROPYTHON

In 'An Introduction To MicroPython' article published in May issue, on page 45, under the subheading 'Loading MicroPython on ESP8266 board,' the first sentence "ESP8266 is a cheap Wi-Fi development board" is incorrect. ESP8266 is an IC, not a development board.

Shashank T.S.
Through email

The author Ayan Pahuja replies:
Depending on the ESP8266 board, it could be a development board or a WLAN module.