

$$I_{OUT(min)} = 1.25V/R18 = 1.25V/130\text{-ohm} = 9.6mA$$

Maximum output current produced by IC6 is calculated using the

relationship:

$$I_{OUT(max)} = 1.25V/R14 = 1.25V/3.3\text{-ohm} = 379mA$$

Table I gives the current pro-

duced by IC6 if you close only one of the switches between S7, S8, S9 and S10.

Heat-sink. IC1 through IC6 are

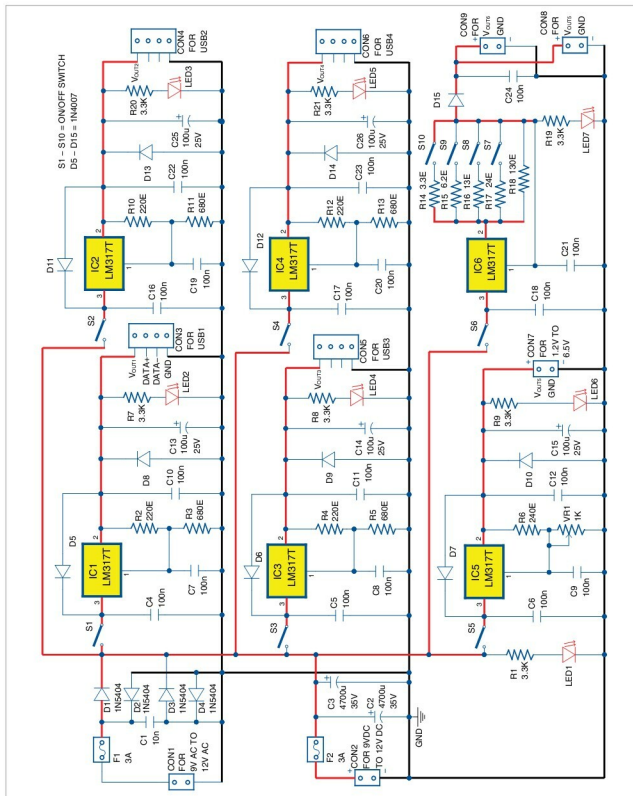


Fig. 1: Circuit diagram of the power supply hub