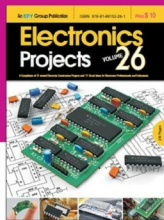


Electronics Projects Vol. 26 is the latest volume in the series, available in digital form.

It is a compilation of 21 construction projects and 71 circuit ideas published in Electronics For You magazine.



This collection of tested circuit ideas and construction projects in a handy volume would interest all classes of electronics enthusiasts—be they students, teachers, hobbyists or professionals!

Electronics Projects Vol. 26 is available on the following digital magazine stores:

- www.lulu.com
- www.magzter.com
- Createspace.com
- www.readwhere.com

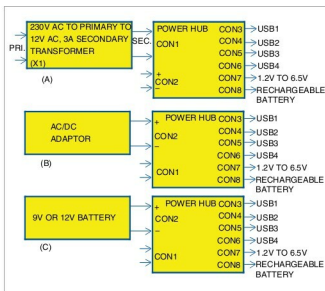


Fig. 2: Power supply hub with quad-USB outputs

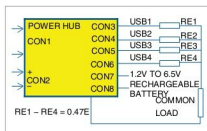


Fig. 3: USB outputs in parallel with equalisation resistors

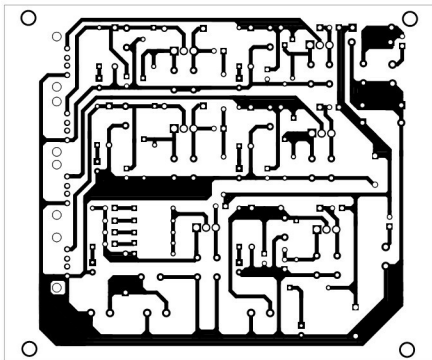


Fig. 4: Actual-size PCB layout of the power supply hub with quad-USB outputs

mounted on individual heat-sinks with thermal resistance below 10°C/W .

Alternatively, IC1 through IC6 can be mounted on a common heat-sink with thermal resistance below 2°C/W , under the condition that these are properly isolated from the common heat-sink.

Input voltages. These are

applied to CON1 or CON2. Fig. 2 shows the following three possible cases for input voltages to the power hub:

1. AC/AC transformer to CON1. CON 2 is not used.
2. AC/DC wall adaptor to CON2. CON 1 is not used.
3. 9V or 12V battery, including car battery, to CON2. CON 1 is not used.