

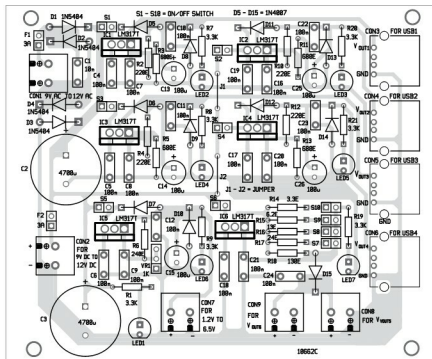


Fig. 5: Component layout of the PCB

You may connect two to four USB outputs in parallel, as shown

in Fig. 3. The condition is to use appropriate equalisation resistors

(RE1 through RE4). In most cases, 0.47-ohm resistors are used.

Construction and testing

An actual-size, single-side PCB for the power supply hub is shown in Fig. 4 and its component layout in Fig. 5. After assembling the circuit on the PCB, enclose it in a suitable box.

The circuit can be connected to a 230V AC primary to 9V/12V, 3A secondary transformer X1 (not shown in Fig. 1). Secondary terminals of X1 should be connected across CON1. You can also use any 9V-12V AC/DC, 3A power adaptor or 9V-12V DC battery. **EFY**



Petre Tzvetan Petrov was a researcher and assistant professor in Technical University of Sofia (Bulgaria) and expert-lecturer in OFPPT(Casablanca), Kingdom of Morocco. Now he is working as an electronics engineer in the private sector in Bulgaria

PCB
POWER

Online PCB Specialist
(Proto and Small Volume)

INTRODUCING
LAYOUT CALCULATOR

Schematic to Gerber File Package

OUR LAYOUT SERVICE

- India's First Online PCB Design Calculator
- Online Calculator
- Cost Effective Solution
- No Exception During PCB Fabrication
- Your Virtual Design Team
- Seamless Flow From Layout To PCB Fabrication

PCB DESIGN SERVICE FROM ₹ 1500

PCB FABRICATION

- PCBs up to 24 Layers.
- Minimum Order Quantity is 1.
- Delivery Starting from 3 working days.
- Impedance Control
- Blind Buried Via

SOLDERINGSOLUTIONS

Circuit Systems India Ltd.
B-24, GIDC Electronics Estate, Sector-25, Gandhinagar-382044, Gujarat, India
Mail: pcb@pcbpower.com | Phone: +91 7600012414/+91 7600012415

www.pcbpower.com

}

20

YEARS OF EXCELLENCE