

Fig. 3: Actual-size, PCB layout of the remote-controlled robot

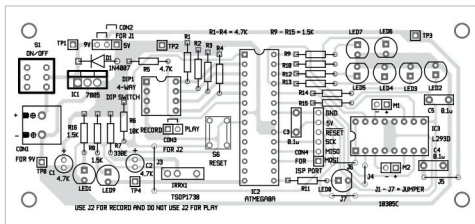


Fig. 4: Components layout of the PCB

the fuse bits to the default value as shown in Fig. 2.

Note. As per datasheet of ATmega-8A, fuse setting 1 means unprogrammed and 0 means programmed.

Construction and testing

An actual-size, single-side PCB layout for the remote-controlled robot is shown in Fig. 3 and its components layout in Fig. 4. After

TABLE II
TEST POINTS

Test point	Details
TP0	0V (GND)
TP1	9V
TP2	5V when S1 is on
TP3	9V/5V based on J1 setting
TP4	LED9 blinks when signal is received from remote

assembling the circuit, place the populated PCB and 9V battery on the chassis of the robot. J1 is used to select 5V or 9V power supply depending on 5V DC motors or 9V DC motors used.

Use of an IC base/socket is recommended for the MCU. Connect M1 and M2 to the PCB through twin-wire external wires. Before running the robot, verify the voltages are as shown in Table II. Your remote-controlled robot is ready to use! **EFY**



Fayaz Hassan is manager at Visakhapatnam Steel Plant, Visakhapatnam, Andhra Pradesh. His interest includes MCU projects, mechatronics and robotics

Read more stories on Components in
www.electronicsb2b.com

TOP COMPONENTS STORIES

- The latest in power converters
- India's leading component distributors
- Growth of Indian electronics components industry
- The latest launches of components for LEDs
- The latest launches of components for electronics

**ELECTRONICS
B2B
INDUSTRY IS AT A**

CLICK OF A BUTTON

Log on to www.electronicsb2b.com and be in touch with the Electronics B2B Fraternity 24x7