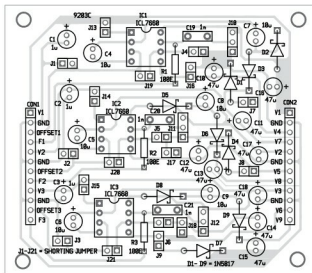


are usually rated at 10 μ F to 100 μ F for 25V or more. Capacitors C16, C17 and C18 are of 47 μ F to 220 μ F for 16V or more. Capacitors C19, C20 and C21 determine the frequencies of internal oscillators. These capacitors can have any appropriate values but the usual values are between 0 μ F and 1nF.

Construction and testing



used in the circuit.

Each IC has seven jumpers that permit it to implement almost all possible application circuits according to the datasheets of the IC. It is recommended to refer datasheets of the ICs before using the circuit.

Capacitors. All capacitors in the circuit should work at high frequencies in switching power supplies. These capacitors depend on the ICs for working frequency and maximum output current, etc. Capacitors C1, C2 and C3 should be of 0.33 μ F to 1 μ F. Capacitors C4 through C15

After proper assembly and configuration with jumpers, the circuit will start working immediately when power is supplied. It has a lot of advantages. For instance, voltages V1, V2 and V3 can be the same or different, and outputs can be paralleled for higher output current. **EPV**




Petre Tzv Petrov was a researcher and assistant professor in Technical University of Sofia (Bulgaria) and expert-lecturer in OFPPT(Casablanca), Kingdom of Morocco. Now he is working as an electronics engineer in the private sector in Bulgaria

Honorarium (minimum ₹1,000)
will be paid to the contributors soon
after publication of their articles.

Complete details may be sent to the
 Editor, Electronics For You,
 D-87/1, Okhla Industrial Area Phase 1,
 New Delhi 110020
 or emailed to editsec@efy.in

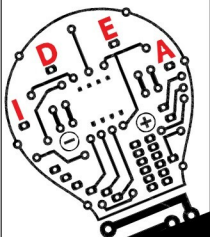For editorial guidelines, visit
<http://efymag.com/Guidelines> for EY authors doc



from designers and
experimenters
for publication in EFY magazine