



4x4x4 LED CUBE

Using AT89C2051

PAMARTHI KANAKARAJA

This 4x4x4 LED cube for use in science laboratories is very easy to assemble. Its LEDs light up in different patterns, creating mesmerising lighting effects.

Circuit and working

Fig. 1 shows the author's prototype of the 4x4x4 LED cube. The complete circuit is shown in Fig. 2. It is built around an AT89C2051 microcontroller (IC2), a 4-to-16 decoder 74HC154 (IC3), four BC547 transistors (T1 through T4) and a few other components. The power supply section is built around a



Fig. 1: Author's prototype

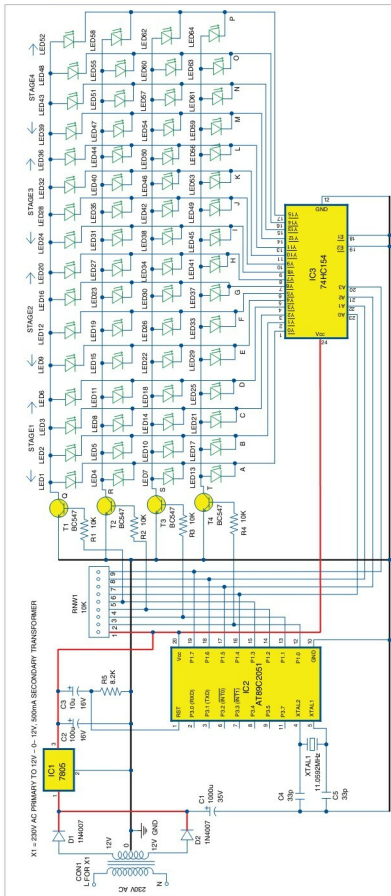


Fig. 2: Circuit diagram of 4x4x4 LED cube using AT89C2051