

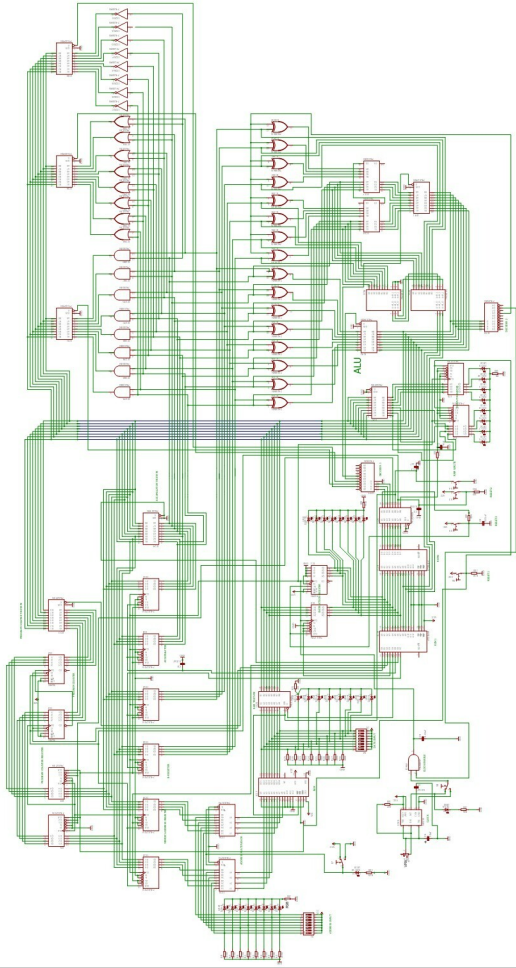


Fig. 2: Circuit of simple 8-bit computer