

High-Fidelity FM TRANSMITTER

JOY MUKHERJI

FM broadcasting is radio broadcasting using frequency modulation technology. In order to attain high-fidelity broadcast of music and speech, all audio frequencies up to 15kHz must be transmitted. The low-power trans-

PARTS LIST

Semiconductors:

IC1	- 74AC74 dual D-type flip-flop with preset and clear
IC2	- 7805, 5V regulator
IC3, IC5	- CD4060 ripple-carry binary counter
IC4	- CD4046 phase-locked loop
IC6	- LM386 low-power audio amplifier
LED1	- 5mm LED
D1	- BB910 varactor diode
T1, T3	- PN2222A npn transistor
T2	- 2N3904 npn transistor

Resistors (all 1/4-watt, $\pm 5\%$ carbon):

R1, R2, R10	- 22-kilo-ohm
R3	- 220-ohm
R4, R5, R6, R9	- 10-kilo-ohm
R7, R12, R13	- 2.2-kilo-ohm
R8, R11, R17, R19	- 100-kilo-ohm
R14	- 47-kilo-ohm
R15, R16	- 33-kilo-ohm
R18	- 330-ohm
VR1	- 470-kilo-ohm potentiometer
VR2	- 10-kilo-ohm potentiometer

Capacitors:

C1, C7, C9-C11, C14, C23	- 100nF ceramic disk
C2	- 330pF ceramic disk
C3	- 10pF ceramic disk
C4	- 2.2pF ceramic disk
C5	- 3pF ceramic disk
C6, C8	- 100 μ F, 25V electrolytic
C12, C20	- 220 μ F, 25V electrolytic
C13	- 22 μ F, 25V electrolytic
C15-C17	- 10 μ F, 25V electrolytic
C18	- 2.2 μ F, 25V electrolytic
C19	- 1000pF ceramic disk
C21, C22	- 22pF ceramic disk
VC1	- 50pF trimmer

Miscellaneous:

RF C1	- 100 μ H, 2-hole balun ferrite core
RF C2, RF C3	- 330 μ H ready-made axial inductor
L1	- 5T 20 SWG 8mm dia. air core spread over 1.2 or 1.5cm. Tap at 1/2T from V+
JACK1, JACK2	- Audio input jacks
XTAL1	- 12MHz crystal oscillator
BATT.1	- 12V battery or 12V DC power supply
ANT.1	- 78cm single-strand wire as antenna

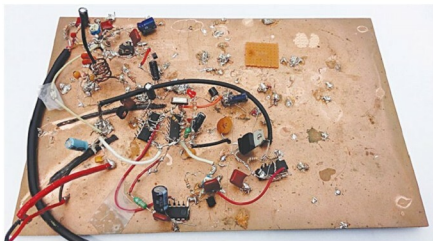


Fig. 1: Author's prototype wired on a copper clad sheet

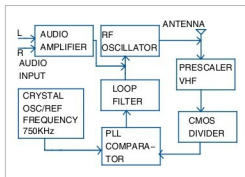


Fig. 2: Block diagram of the high-fidelity FM transmitter

Circuit and working

The author's prototype of the high-fidelity FM transmitter circuit wired on a copper clad sheet is shown in Fig. 1. Block diagram and circuit are shown in Figs 2 and 3, respectively. The circuit is built around dual D-type positive-edge-triggered flip-flop 74AC74 (IC1), ripple-carry binary counter CD4060 (IC3 and IC5), low-power audio amplifier LM386 (IC6), phase-locked loop CD4046 (IC4), 5V voltage regulator 7805 (IC2) and a few other components.

Transistor T1 along with resistors R1, R2 and R3, capacitors C2 and C5, coil L1, trimmer capacitor VC1, and varactor diode D1 forms a voltage-controlled oscillator (VCO) in Pierce configuration. IC1 acts as a VHF prescaler and divides the oscillator frequency by a factor of 4. Low-level RF output is taken via half-turn tap off L1 and fed to pin 3 of IC1 via C3 and to antenna via C4. The 24MHz (96MHz/4) output from the prescaler is further divided by 32 by binary counter IC3. This

Test Points

Test point	Details
TP0	0V (GND)
TP1	12V
TP2	5V
TP3	Amplified audio signal
TP4	3.6V-4.2V
RF OUT	96MHz
LED1	'On' when frequency is locked

mitter presented here achieves that using simple and readily available components. Its output frequency is locked to 96MHz using the phase-locked loop (PLL) approach.