



Pin 13 of IC4 is coupled to a long time-constant filter formed by R10 and C16. C16 charges to the average DC voltage and so provides a control voltage to the transmitter's oscillator

The error signal from pin 13 of IC4 is filtered and coupled back to the varactor diode to correct the frequency. In effect, the oscillator is stabilised and referenced to a

The stereo audio input is taken from audio jacks JACK1 and JACK2