

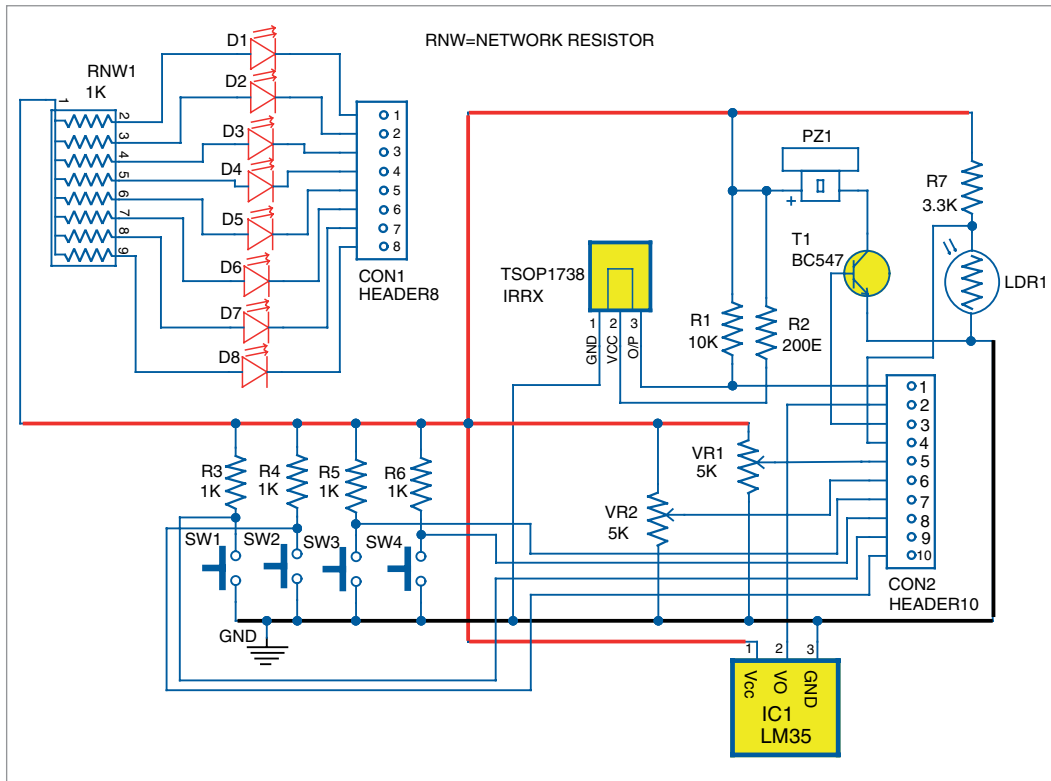


Fig. 8: Circuit diagram of DAIO module

of DAIO module to NodeMCU board. The Vcc terminal of DAIO module should be connected to 3.3V and its ground pin to ground pin of NodeMCU board. **EFY**



Dr C.H. Vithalani is professor in Electronics and Communication Engineering Department at Government Engineering College, Rajkot (Gujarat). He has guided 16 PhD scholars and published 25 research papers. Solving real-life challenges by mentoring innovative student projects is his hobby

India's 1st Independent Survey



For details www.efy.in/elcina-imrb



electronics
YOURS SINCE 1969 FOR YOU