

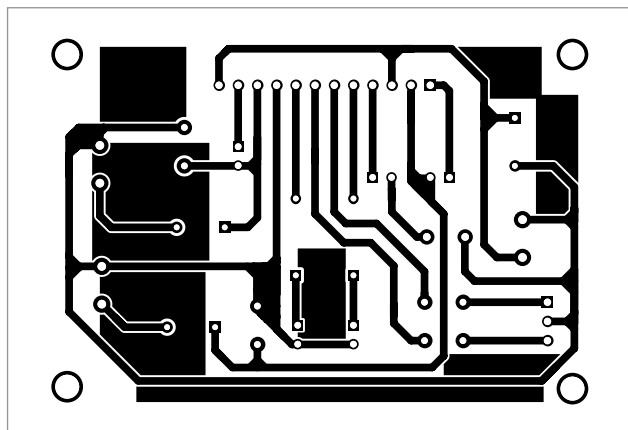


Fig. 3: Actual-size PCB layout for the amplifier

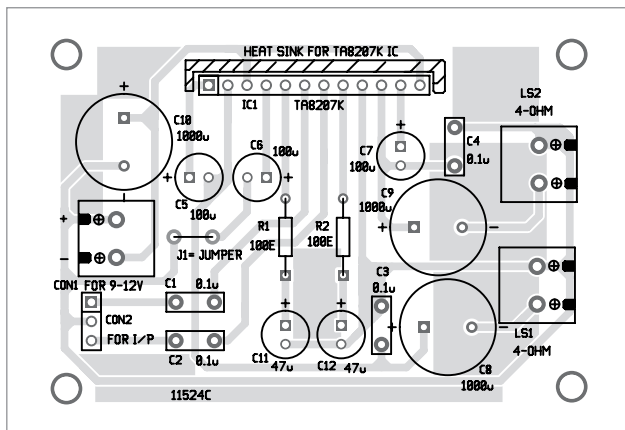


Fig. 4: Components layout of the PCB

After assembling the circuit, connect audio input from your source (MP3 player, computer, mobile phone, etc) across CON2 and two speakers across LS1 and LS2. Connect the 12V battery across CON1.

Calibration and adjustment

You may use a signal generator for calibration and adjustments. If you do not have a signal generator, you may use a small metal screwdriver for testing.

To test, connect the 12V battery and the two speakers to the amplifier. Pick up the screwdriver and touch it gently on any of the inputs at 3-pin connector (CON2); you should hear a humming sound coming from the speakers.

If you have a signal generator, you can switch it to 1kHz frequency and touch its probe to left and right input points of the amplifier one by one. You should hear an amplified audio

tone from the speakers.

Now you may connect audio output of your source of signal to CON2 and enjoy noise-free amplified music. **EFY**



Raj K. Gorkhali is an electronics hobbyist and a regular contributor to EFY

“ I started reading it when I was a student...
...and I am still reading it, as a student ”

—CEO, Design House

electronics
FOR YOU
YOURS SINCE 1969

India's
No.1
Electronics
Magazine
RANKING AS PER
ELCINA-IMRB
REPORT



To Subscribe:
<https://subscribe.efy.in>

OR

Scan This Code



For any query, call: 011-4059 6600 or email: support@efy.in