



Single-Channel Audio Amplifier

Raj K. Gorkhali

Here is a simple single-channel audio amplifier that can be made using IC LM380N. As per the datasheet, LM380N delivers an output of 2.5 watts with an 18V power supply and an 8-ohm speaker. This project was tested using a 12V DC power supply.

The power supply can be 230V to 12V DC adaptor or a 12V battery. But

a 12V battery would be better as an AC/DC adaptor may cause humming noise. The LM380N is an inexpensive 14-pin PDIP IC that is easily available in the market.

Circuit and working

Circuit diagram of the audio amplifier is shown in Fig. 1. A suitable pot (VR1) is connected at input pin 2 of the IC. An

8-ohm, 3-watt speaker is connected to IC's pin 8 through 470µF electrolytic capacitor C6. IC's pin 14 is connected to positive terminal of 12V supply.

Audio input is given to pin 2 of IC1 through 4.7µF electrolytic capacitor C1 and pot VR1 that is used for volume control. Pins 3 through 7 and pins 10 through 12 of IC1 are all connected to ground. Pins 9 and 13 are not connected.

Construction and testing

An actual-size PCB layout for the amplifier is shown in Fig. 2 and its component layout in Fig. 3. A suitable Veroboard can be used in place of the PCB.

PARTS LIST

Semiconductors:

IC1 - LM380N audio amplifier

Resistors (all 1/4-watt, ±5% carbon):

R1 - 2.2-ohm

VR1 - 10-kilo-ohm pot

Capacitors:

C1 - 4.7µF, 35V electrolytic

C2 - 470pF ceramic disc

C3 - 0.22µF ceramic disc

C4, C6 - 470µF, 35V electrolytic

C5, C7 - 0.1µF ceramic disc

Miscellaneous:

CON1 - 2-pin terminal connector

CON2 - 2-pin connector

LS1 - 8-ohm, 3W speaker

- Heat-sink for IC1

- 12V power supply/ 12V battery

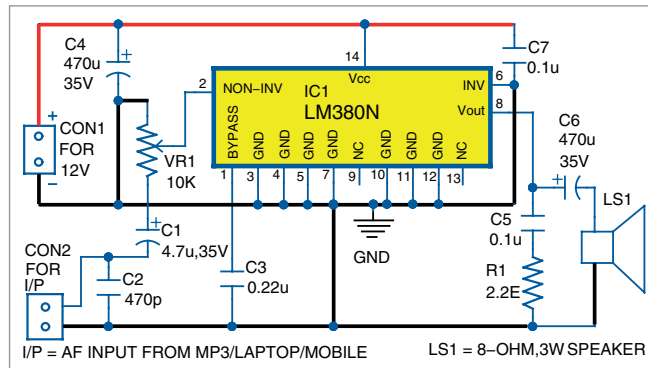


Fig. 1: Circuit diagram of the amplifier

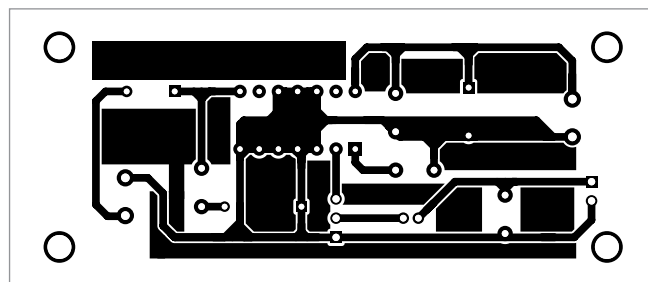


Fig. 2: Actual-size PCB layout for the amplifier circuit

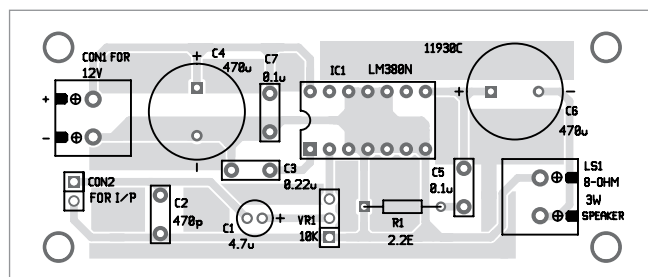


Fig. 3: Component layout of the PCB