

OVERVOLTAGE And UNDERVOLTAGE PROTECTION For Electrical Appliances

SHAMAIL AHMAD

In some places, especially in developing countries like ours, sudden ups and downs in the mains voltage are quite common. This sometimes causes a serious failure of electrical appliances like television sets, air-conditioners, and refrigerators, which are not designed to tolerate lower or higher voltages beyond a small limit.

This circuit incorporates a low-voltage and high-voltage tripping mechanism to protect the appliances from any damage due to voltage fluctuation.

The author's prototype on breadboard is shown in Fig. 1. The circuit diagram is shown in Fig. 2.

The circuit's dual power supply using transformer X1 and diodes D1 through D4 isolates the supply between relay RL1 and control circuitry with the help of optocoupler IC PC817. It helps to eliminate the voltage-dropping problem when the relay energises. The capacitors C1, C2, and C3 are used to smoothen the rectified pulsating DC from the diodes.

The ICs IC1 and IC2 (TL431) are adjustable shunt regulators. The R1-R2 resistor voltage divider network is used to set the upper cut-off voltage and preset VR1 is used to set the lower cut-off voltage. Diode D5 works as a freewheeling diode and transistor T1 is used to drive

PARTS LIST

Semiconductors:

- IC1, IC2 - TL431 shunt regulator
- IC3 - PC817 optocoupler
- D1-D5 - 1N4007 rectifier diode
- T1 - BC337 npn transistor

Resistors (all 1/4-watt, $\pm 5\%$ carbon), unless stated otherwise:

- R1 - 9-kilo-ohm
- R2 - 1.2-kilo-ohm
- R3 - 1-kilo-ohm
- R4 - 4.7-kilo-ohm, 0.5W
- R5 - 10-kilo-ohm
- R6 - 1-kilo-ohm
- VR1 - 10-kilo-ohm preset

Capacitors:

- C1, C2 - 100 μ F, 35V electrolytic
- C3 - 1000 μ F, 35V electrolytic

Miscellaneous:

- X1 - 230V AC primary to 12V-0-12V, 500mA secondary
- RL1 - 12V single changeover relay
- CON1, CON2 - 2-pin terminal connector
- 3-pin terminal connector

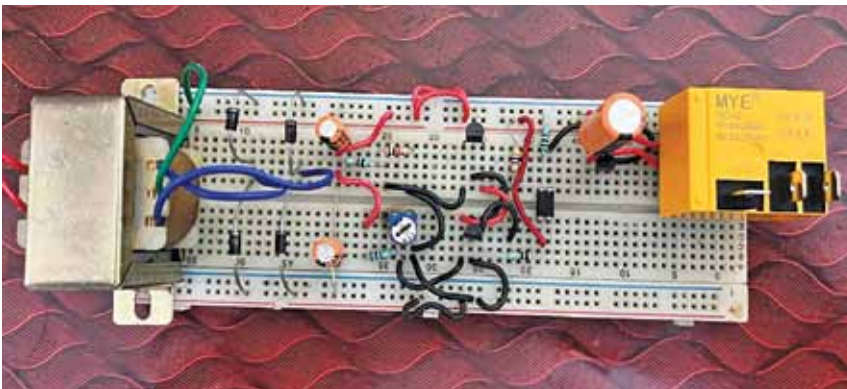


Fig. 1: Author's prototype on breadboard

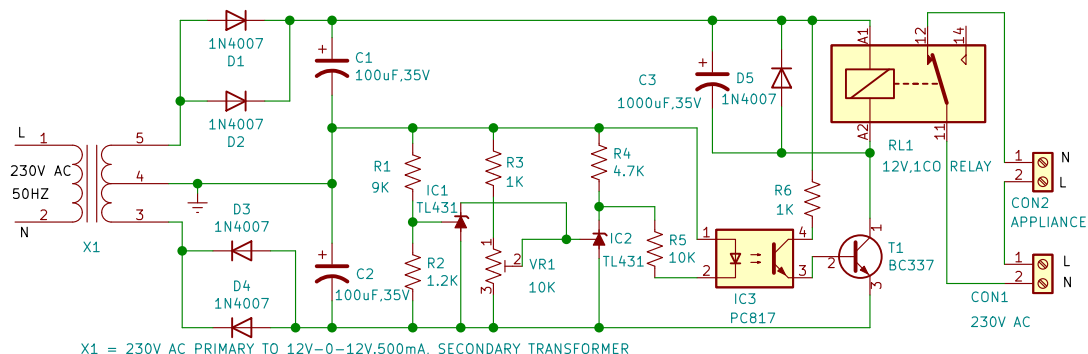


Fig. 2: Circuit diagram