

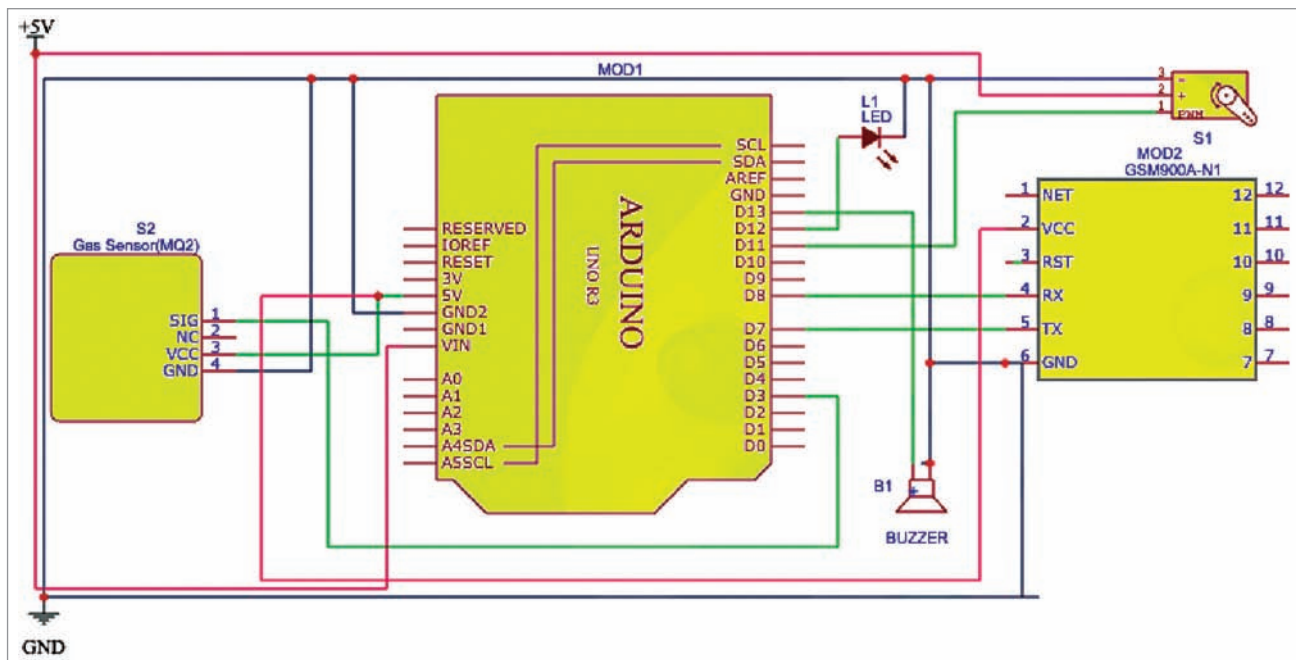


Fig. 4: Arduino connection with buzzer and LED

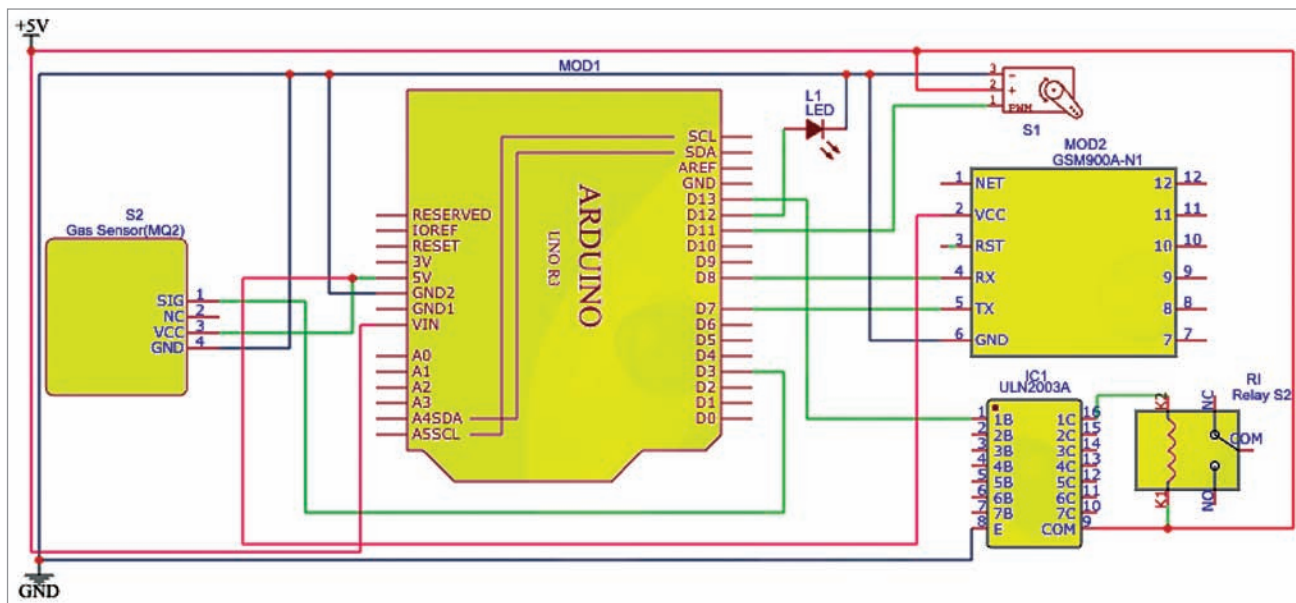


Fig. 5: Circuit with relay driver ULN2003 and relay

its joints.

Blockages in the burner or defective regulators can also cause gas leaks. LPG is highly combustible when mixed with air. When gas leaks inside a confined space such as a house/kitchen, an explosion may occur if there is a source of

ignition. Therefore, gas leakage is very dangerous.

This project aims to provide protection for homes/hotels/restaurants from the aforementioned problems and their adverse effects. The author's prototype is shown in Fig. 1, while the block diagram is shown in

Fig. 2. The required components for the project are listed in the Bill of Material table.

Software

The Arduino IDE is used here to create the code. In the code, first, include the SoftwareSerial library