

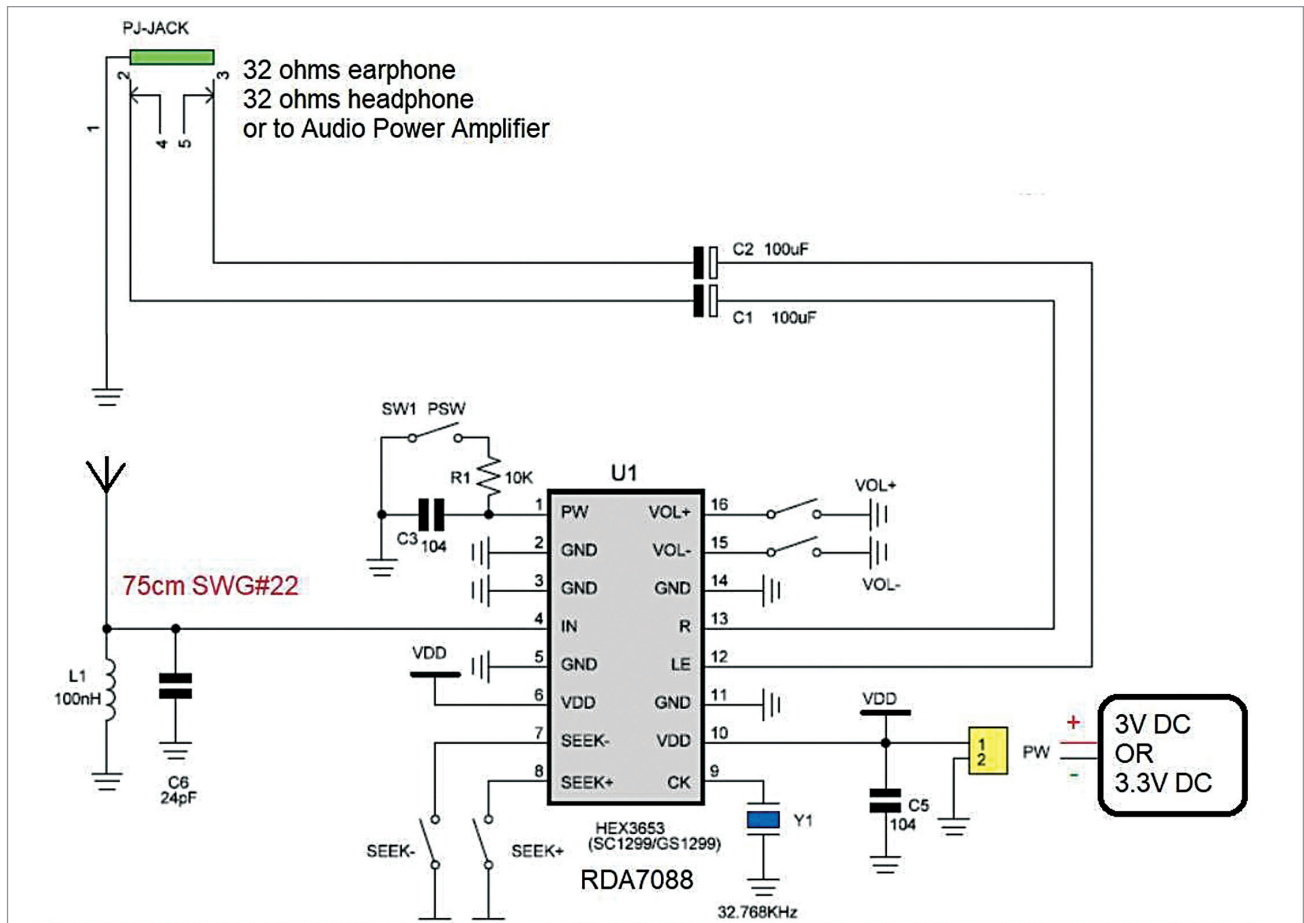


Fig. 2: Circuit diagram

Provide 3V DC from two 1.5V AA-type cells connected in series. Ensure polarity of the power source is right while connecting the battery to the circuit. Instead, you can also provide 3.3V DC from a 5V adaptor. The earphone or headphone wire can also work as FM input antenna.

Try the following functions to ensure that the circuit is working properly:

1. Power on/off control using SW1 (PSW) is a toggle type input. Pressing once turns the radio on. Pressing again turns the radio off.
2. Pressing SEEK- searches the next

available channel towards 76MHz.

3. Pressing SEEK+ searches the next available channel towards 108MHz.

4. Pressing VOL- reduces the volume.

5. Pressing VOL+ increases the volume.

Depending on the signal strength, the automatic gain control provides consistent performance with reduced noise. The overall performance of the FM stereo receiver is good compared to the cost and number of components required. **EFY**

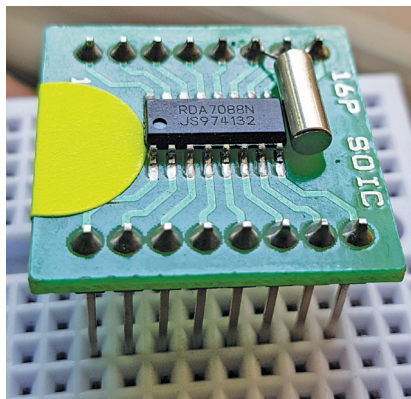


Fig. 3: FM RDA7088 IC mounting

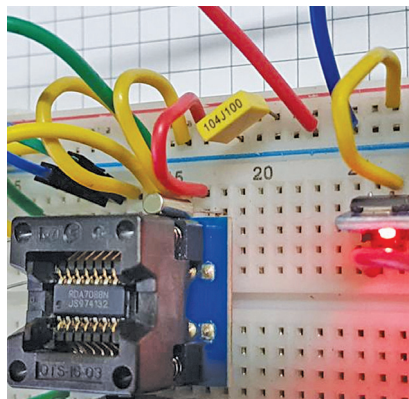


Fig. 4: IC connection on breadboard

The author K.N. Antony, with a B.Sc. degree in physics and a B.Tech degree in electronics, holds several US patents and is author of many international publications, including WIPO. His hobbies include RF and audio amplifier design