



DO-IT-YOURSELF: CIRCUIT IDEA

emitter to collector of T1. As lesser current passes through LM317 and most of the current flows through

T1, heatsink of IC1 is less warm as compared to the heat sink of transistor T1 heat sink. So the heat sink for

T1 needs to be bigger than the heat sink for IC2 and IC3. Use of exhaust fan helps in proper dissipation of

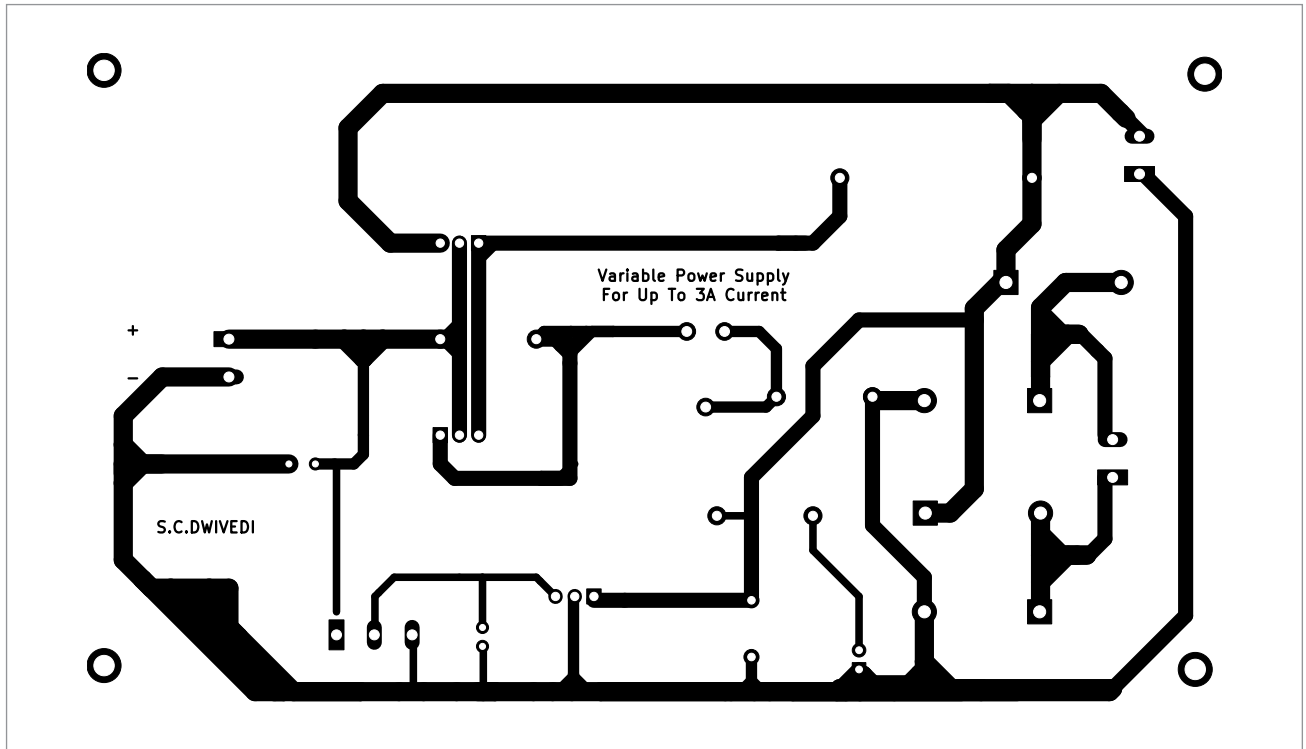


Fig. 4: Actual-size single-side PCB layout

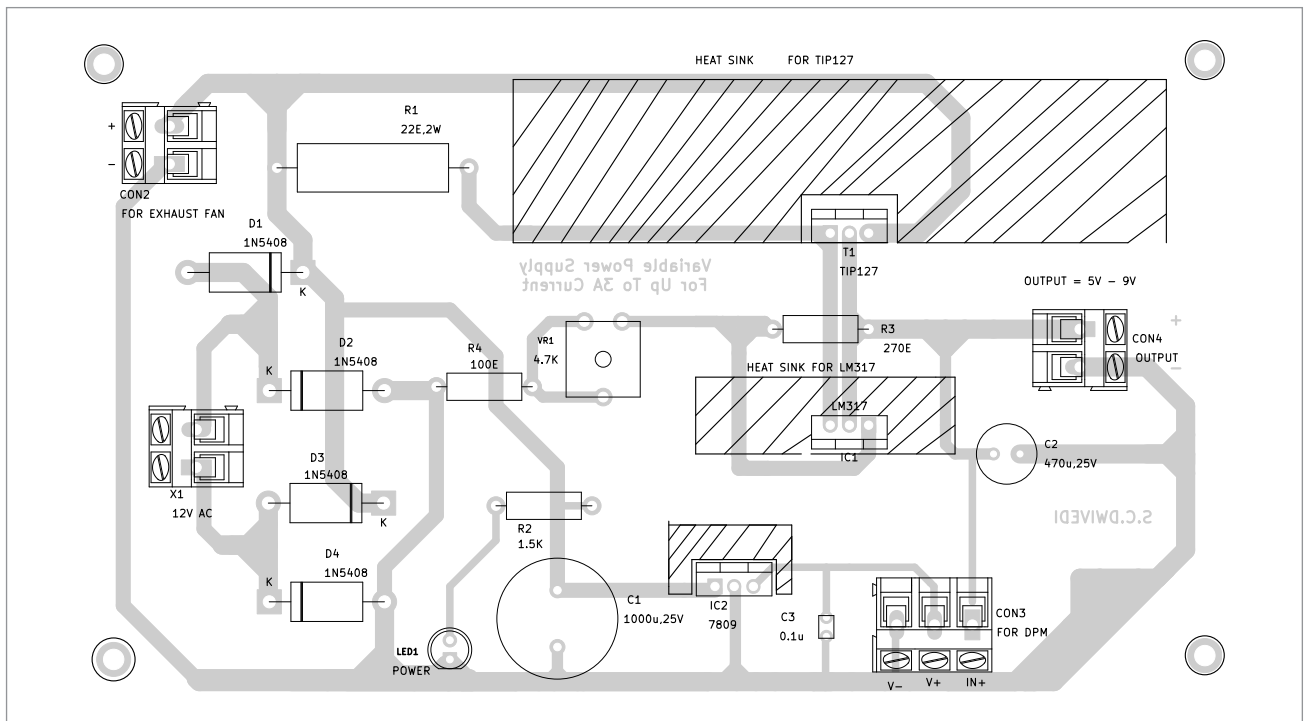


Fig. 5: Component layout