

SINUSOIDAL SIGNAL GENERATOR With Forward And Inverted Outputs

PETRE TZV PETROV

During the testing of audio systems and telephone-like systems, it is useful to have a sinusoidal signal generator that produces forward and inverted signals in the range of around 15Hz to 15kHz. Here is one possible way of making that signal generator.

This signal generator can also be used as a sine wave oscillator, a telephone amplifier, or a low-frequen-

FREQUENCIES SELECTION

Range	Closed switches	Resistors using potmeters VR1 and VR2	Capacitors	Approximate frequency
1	S1A1+S1B1	11.47k	10nF	1.4kHz
	S1A1+S1B1	0.47k	10nF	16kHz
2	S2A1+S2B1	11.47k	100nF	140Hz
	S2A1+S2B1	0.47k	100nF	1.6kHz
3	S3A1+S3B1	11.47k	1μF	14Hz
	S3A1+S3B1	0.47k	1μF	160kHz

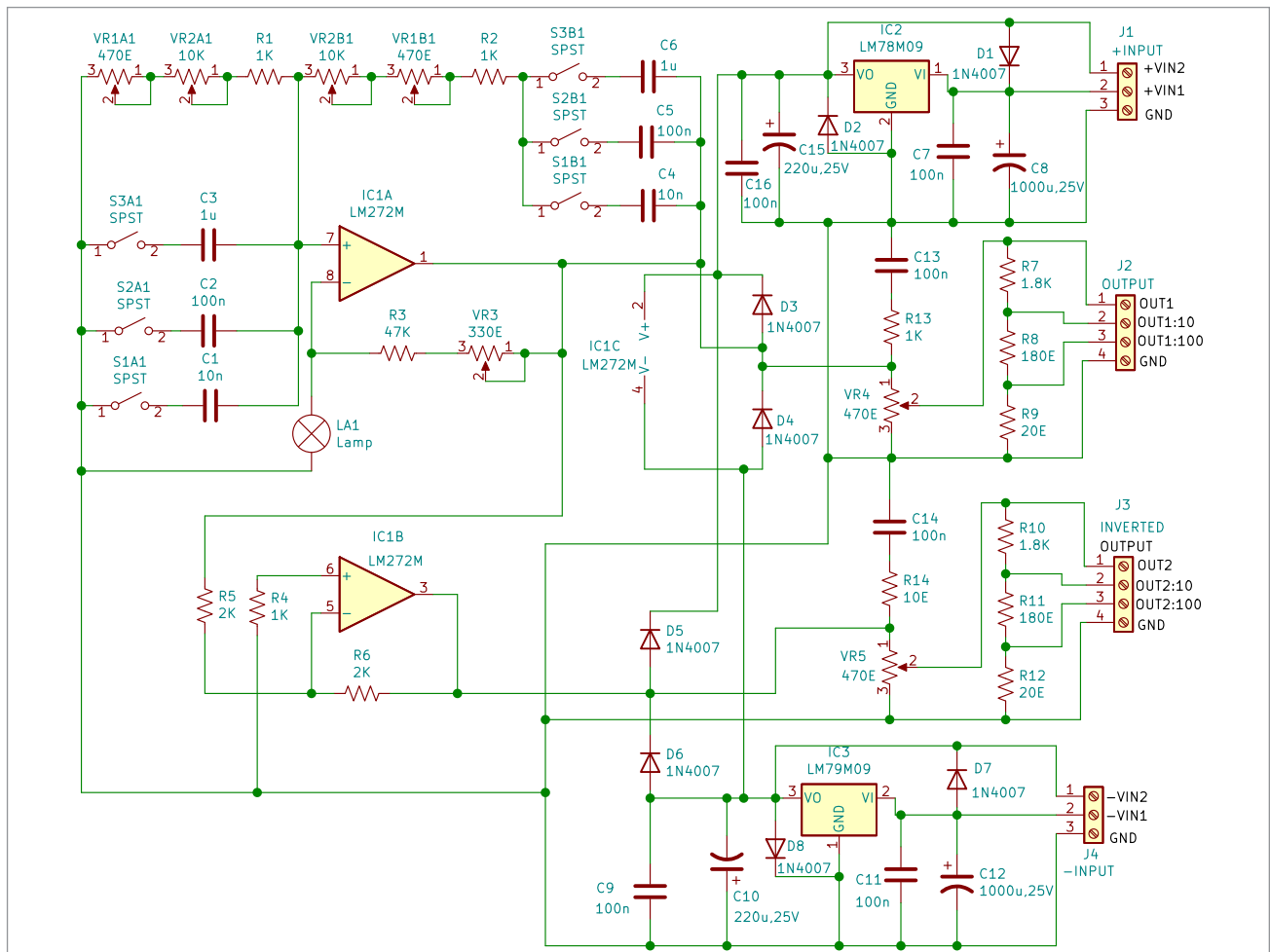


Fig. 1: Circuit diagram