

S.C. DWIVEDI

Room heaters also consume lots of electricity, unnecessarily, when not required, as these have high wattage rating. This simple but useful circuit can help avoid all such issues. It can control up to two heat convectors.

IC CD4060 requires external timing components to feed oscillations to the clock at pin 11. The timing capacitor is connected to

The circuit uses only four outputs: Q3 (pin 7), Q11 (pin 1), Q12 (pin 2), and Q13 (pin 3). Output pin 7 is used to flash LED4 for indicating that the circuit is oscillating. Output pin 1 is used to connect heat convactor HC1 via relay driver transistor T1. LED1 and R4 are

