

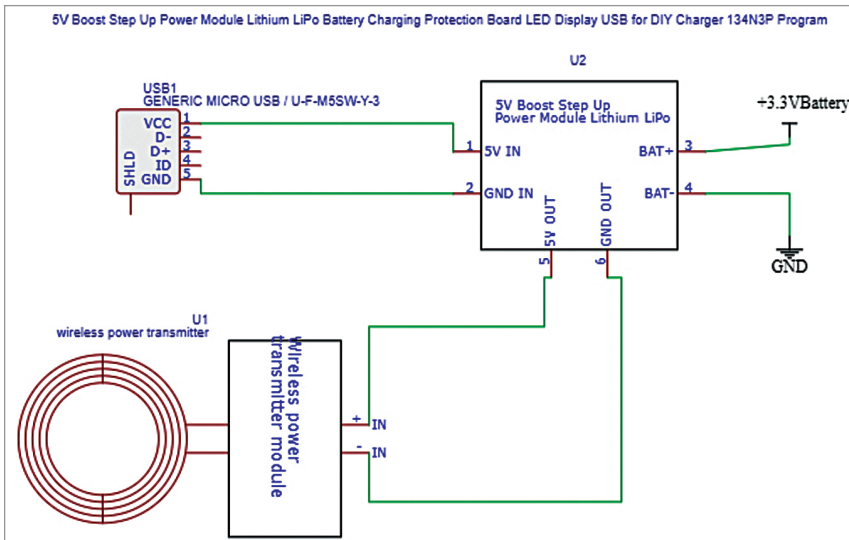


Fig. 10: The circuit diagram

charging module have to fit inside the case, which has to be cut to make provision for input power charging (USB) and output power. A cavity is also made on one wall of the case for the coil and MagSafe magnet to be placed, as shown in Fig. 3.

For the circuit, we can either use a 5V step-up battery management IC or a module. A TP4056 one-ampere battery charging module was used in the author's prototype. The module's output is connected to a wireless transmitter, as shown in Fig. 5.

Connections

The battery terminals are soldered

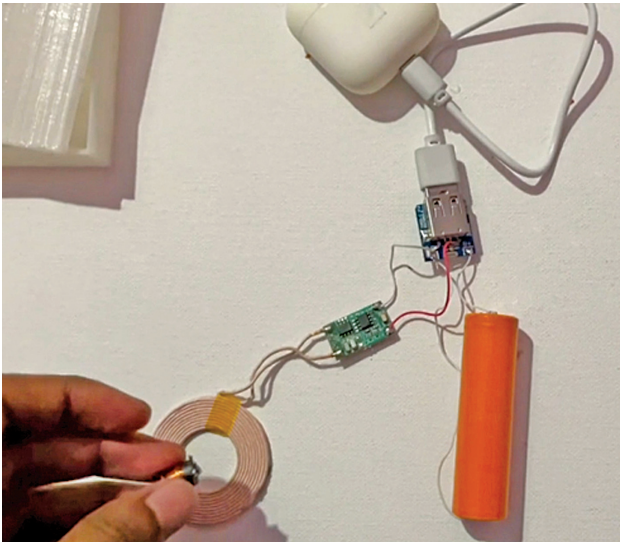


Fig. 11: Fixing the coil and magnet



Fig. 13: An inside view

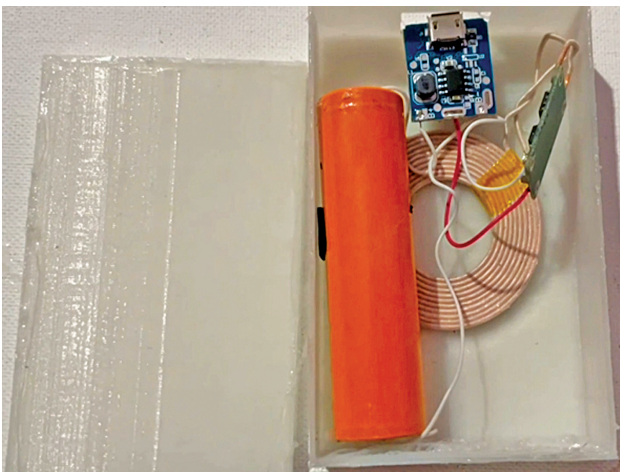


Fig. 12: Fixing the coil and circuit along with battery

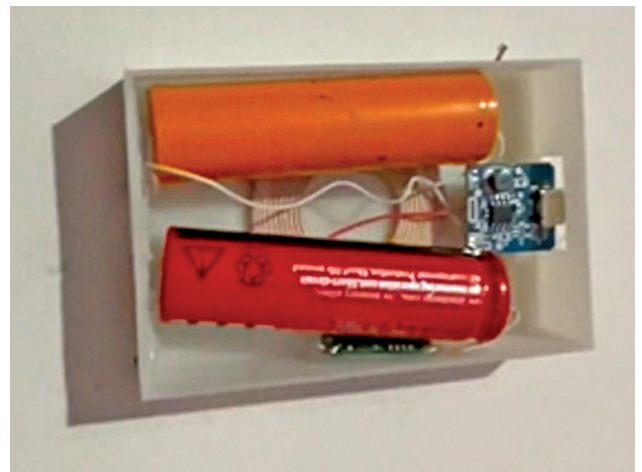


Fig. 14: Author's prototype without the top cover