

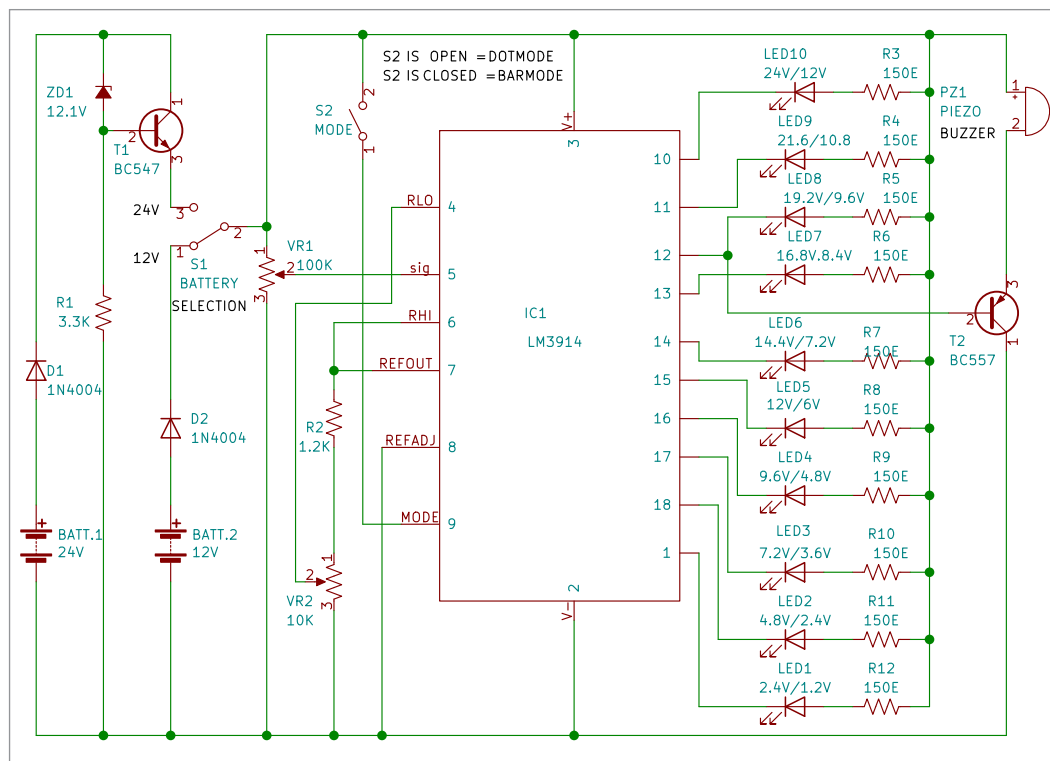


Fig. 3: Circuit diagram

sistor T1 to reduce the 24V battery voltage to 12V. Pin 3 of IC1 is connected to positive side of 12V to operate the circuit while its pin 2 is connected to ground.

To check voltage level of the battery, use two crocodile clips with about 30cm long wires soldered to each. One of the clips could be red with red wire soldered to it and the other black with black wire soldered to it. Connect red clip to positive terminal of the battery under test and

Looking for Business Opportunity?

BECOME A DEALER FOR INDIA'S LEADING EDUCATIONAL KITS BRAND

A WIDE RANGE OF ELECTRONICS KITS AND TRAINING MATERIAL FOR ENGINEERING STUDENTS, ENGINEERS, HOBBYISTS, COLLEGE LABS & TRAINING INSTITUTES

Find Our Dealer Near You: kitsnspares.com/dealers

Interested? Call Shyam (8800100761)

To view our entire range of products, visit our website: www.kitsnspares.com

kitsnspares
For the 'engineer' in you

kitsnspares.com D-87/1, Okhla Industrial Area, Phase 1, New Delhi 110020
Phone: +91-11-26371661 • E-Mail: info@kitsnspares.com



SUPPLIERS INVITED
If you want to sell through our network