

www.efy.in

EFY GROUP
YOURS SINCE 1969

“

Branding is what people say about you when you are not in the room.

”



-Jeff Bezos

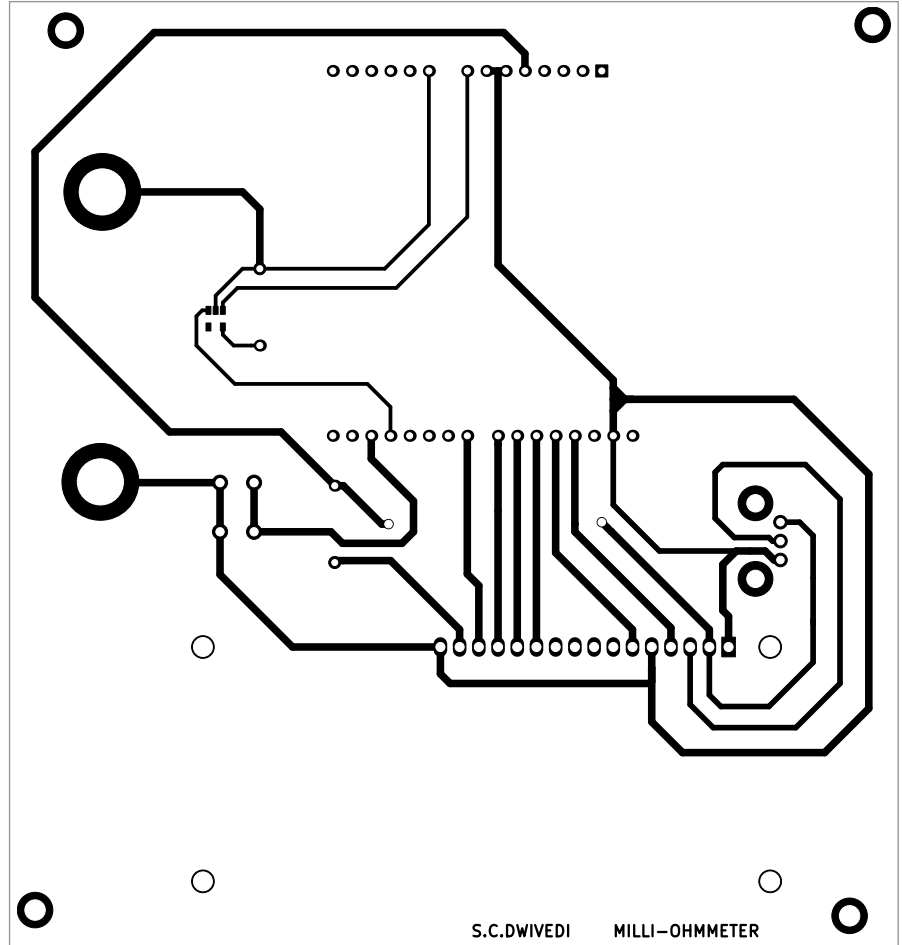


Fig. 3: Actual-size single side for milli-ohm meter

should not be more than one ohm. If it is more than one ohm, '!OL OR NC!' message will appear on the LCD1.

Also, whenever the resistance value is beyond the one-ohm limit,

it is disconnected from the circuit. If S1 is pressed again after measurement, IC1 is disabled.

Arduino Uno is a popular open source microcontroller development board based on Atmega328P microcontroller. It has fourteen digital input/output (I/O) pins of which six can be used for PWM outputs and six for analogue inputs. A 16MHz crystal, USB connector, power jack, and ICSP header can also be connected to it. It comes with preloaded Arduino bootloader, so there is no need of additional hardware to burn the Atmega chip.

The circuit uses the software program loaded into the internal memory of Arduino Uno for operation. The program mR_Meter.ino is written in Arduino programming language known as Sketch. An

PARTS LIST

Semiconductors:

- Board1 - Arduino Uno
- IC1 - MIC5219 low dropout regulator

Resistors (all 1/4-watt, $\pm 5\%$ carbon):

- R1 - 33-ohm
- R2 - 150-ohm
- R3 - 10-kilo-ohm
- VR1 - 10-kilo-ohm pot/preset

Miscellaneous:

- LCD1 - 16x2 LCD
- S1 - Push-to-on switch
- Test probes
- Jumper wire
- 9V battery or 9V, 500mA adaptor
- Resistance below 1-ohm (say, 680milli-ohm)