

Automatic STREETLIGHT CIRCUIT

S.C. DWIVEDI

Often streetlights remain on till late in the morning and are not switched on as soon as it gets dark. This circuit will automatically turn off a streetlight at dawn every morning and switch it on again at dusk each evening. The author's prototype is shown in Fig. 1 while its circuit diagram is shown in Fig. 2.

The circuit has a step-down transformer (X1), a bridge rectifier (BR1), 12V voltage regulator 7812 (IC1), op-amp LM741 (IC2), a 12V single-changeover relay (RL1), and a few other components. Capacitor C1 connected across the supply terminals minimises ripples and any other noise signals.

The circuit works on 12V DC, which is obtained from the 230V AC primary to 15V, 500mA step-down transformer X1. The 230V AC mains

is connected to the primary of X1 via CON1 in the circuit. The transformer's 15V AC secondary is connected to bridge rectifier BR1 for rectification of the voltage, which is filtered by capacitor C1. The rectified and filtered voltage goes to IC LM7812 to get regulated 12V DC voltage for the circuit.

Heart of the circuit is op-amp LM741 in 8-pin DIP package. Here it is used as a comparator and not as an amplifier. It compares the input voltage (V_{in}) with the reference voltage (V_{ref}). When V_{in} rises above or falls below V_{ref} , the output changes accordingly.

The reference voltage V_{ref} is provided at inverting input (pin 2) of the IC through divider network built around resistor R2, pot VR1, and resistor R3. The input voltage goes to the IC's non-inverting input (pin 3) through the divider network comprising resistor R4 and light-dependent resistor LDR1. Pot VR1 is used for setting the reference voltage.

Light-dependent resistor is a special type of

resistor whose value changes with the intensity (brightness) of light falling on it. It has resistance of about 1-mega-ohm when in total darkness, but a resistance of only a few kilo-ohms in bright sunlight. It responds to a large part of the light's spectrum.

Working of the circuit is simple. As soon as power is switched on, LED1 glows. In daytime, when light falls on LDR1, the input voltage at pin 3 of IC2 is low as compared to the reference voltage at pin 2, so out-

PARTS LIST

Semiconductors:

- IC1 - LM7812, 12V voltage regulator
- IC2 - LM741 op-amp
- T1 - 2N2222 NPN transistor
- BR1 - 1A bridge rectifier
- D1 - 1N4007 rectifier diode
- LED1 - 5mm LED

Resistors (all 1/4-watt, $\pm 5\%$ carbon):

- R1, R2, R4, R5 - 1-kilo-ohm
- R3 - 470-ohm
- R6 - 3.3-kilo-ohm
- VR1 - 2.2-kilo-ohm pot

Capacitors:

- C1 - 1000 μ F, 35V electrolytic
- C2 - 100 μ F, 35V electrolytic

Miscellaneous:

- CON1, CON2 - 2-pin connector
- RL1 - 12V, 1C/O relay
- X1 - 230V AC primary to 15V, 500mA secondary transformer
- 500W, 230V streetlight

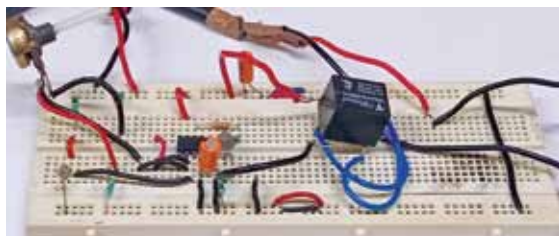


Fig. 1: Author's prototype tested on a breadboard

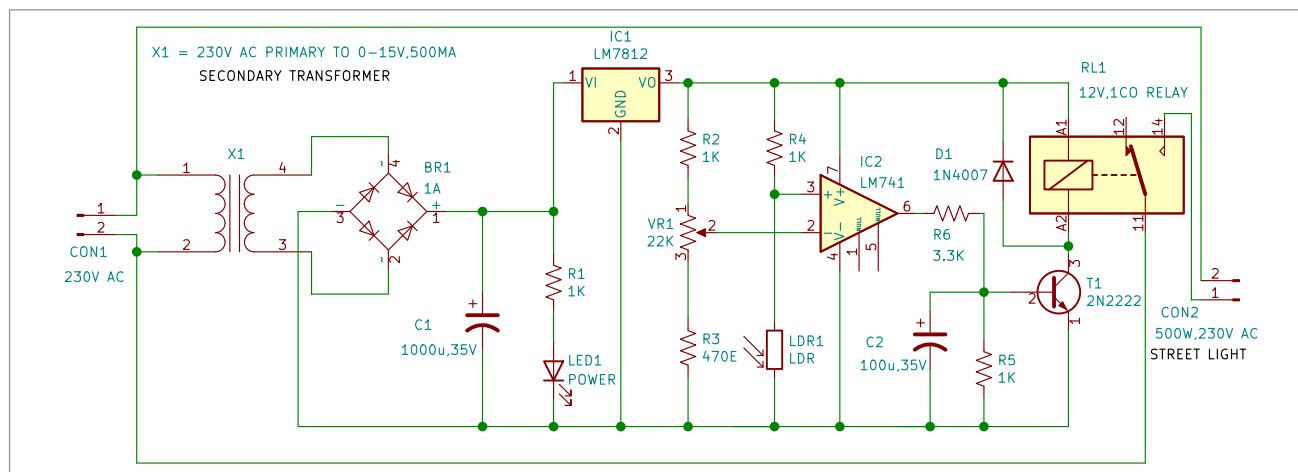


Fig. 2: Circuit diagram for the automatic streetlight