

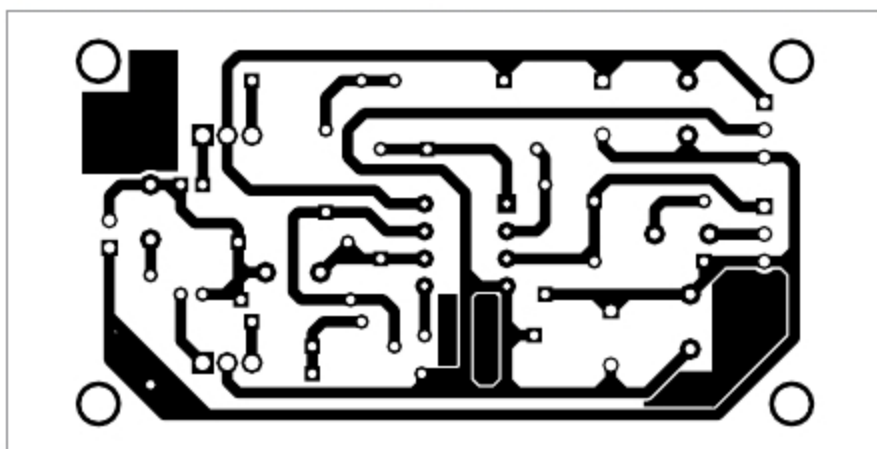


Fig. 2: Actual-size PCB layout of the universal circuit

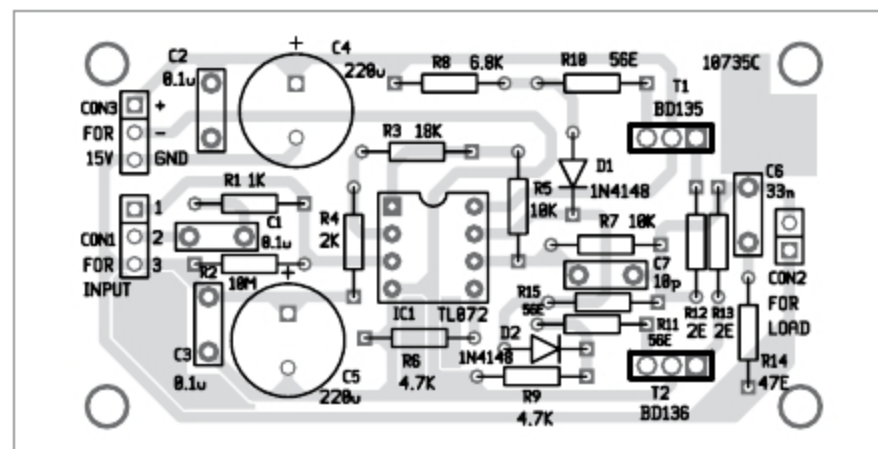


Fig. 3: Components layout for the PCB

tor R15 should have the minimum applicable value to have minimal THD and IMD.

Resistors R12 and R13 operate as current-limiting elements. Maximum output current is determined by the following relationship:

$$I_{max} = 0.68V/R12 = 0.68V/R13 = 340mA$$

R10, R11, C6 and R14 reduce THD and increase stability of the circuit.

Construction and testing

An actual-size PCB layout of the circuit is shown in Fig. 3 and its components

layout in Fig. 4. After assembling the circuit on the PCB, connect a $\pm 15V$ power supply across CON3.

You can give three types of inputs—DC, AC and audio—across CON1. Connect DC input across terminals 1 and 3 of CON1, or AC input across terminals 2 and 3 of CON1. Connect audio signal input from the mobile/laptop/PC across terminals 2 and 3 of CON1.

The circuit can be tested with a resistive load of 100-ohm connected across CON2 using a power supply of $\pm 15V$ and AC input signal of $\pm 1V_{pp}$,

which should give a total gain of -10. The circuit does not require any adjustment. You may need small heat-sinks for T1 and T2 with thermal resistance around $35^{\circ}C/W$. **EFY**



Petre Tzv Petrov was a researcher and assistant professor in Technical University of Sofia, Bulgaria and expert-lecturer in OFPPT (Casablanca), Kingdom of Morocco. Now he is working as an electronics engineer in the private sector in Bulgaria

support@efy.in

Do you have a query, suggestion or a complaint?

You can e-mail it to support@efy.in and we will take care of the rest.



electronics
FOR YOU
www.efymag.com

ELECTRONICS
BAZAAR
https://ebmag.biz

OpenSource
THE COMPLETE MAGAZINE ON OPEN SOURCE
www.opensourceforu.com

EFYGROUP
YOURS SINCE 1999
www.efy.in