

This Stereo Amplifier Is Simple To Make

Raj K. Gorkhali

Here is a simple stereo amplifier you can make with a CD6283 audio amplifier and a few passive components. It provides an output of 4.6 watts per channel with a 12V power supply.

Circuit diagram of the stereo amplifier is shown in Fig. 1. CON1 is the connector for 6-12V input power supply, CON2 is for the input signal

and CON3 provides the output to two speakers that may be connected to it.

Pins 5 and 7 of IC1 are connected to CON2 for audio inputs via capacitors C2 and C3, respectively. Pin 12 is connected to CON1 connector for power supply. Pin 2 of IC1 is connected to left (L) channel output via electrolytic capacitor C10 and pin 10 of IC1 is connected to right (R) chan-

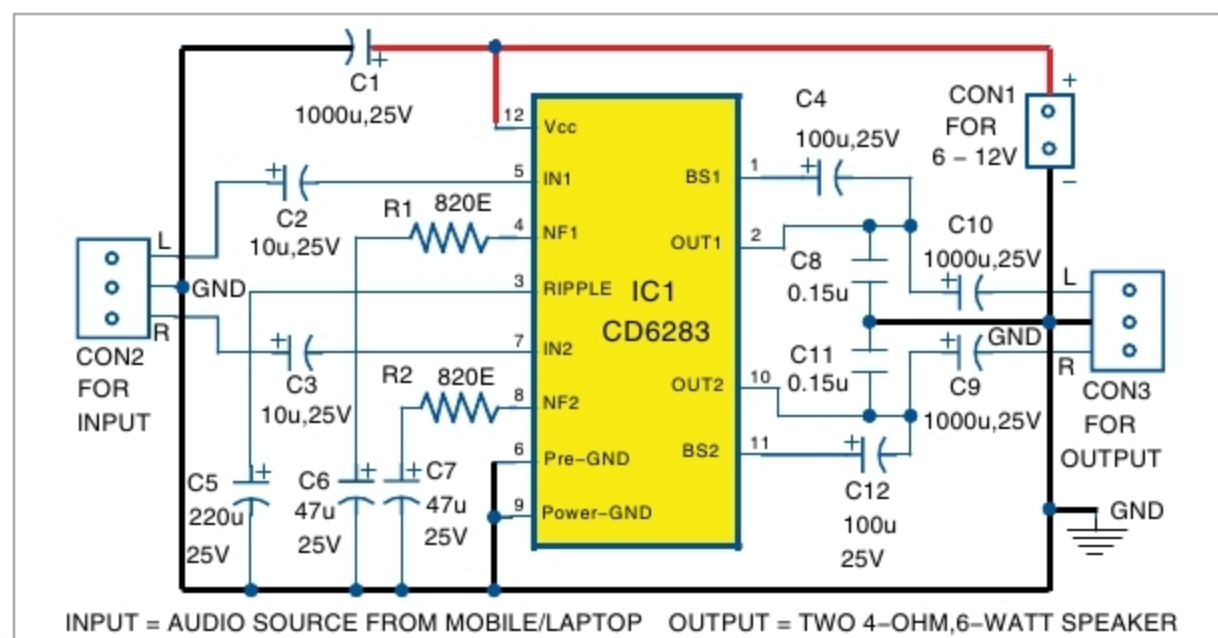


Fig. 1: Circuit diagram of the stereo amplifier

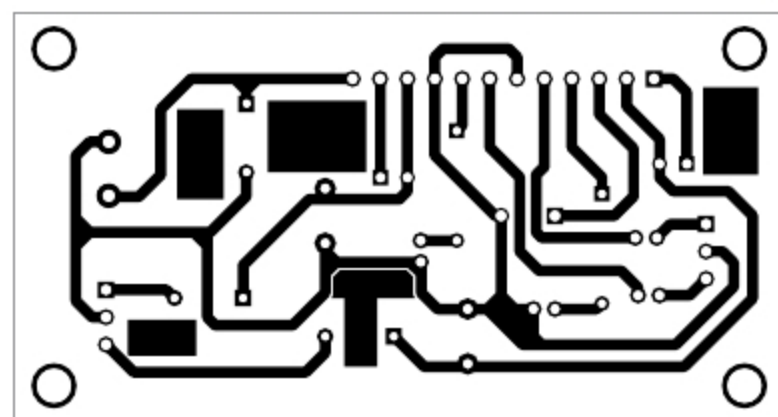


Fig. 2: Actual-size PCB layout for the stereo amplifier

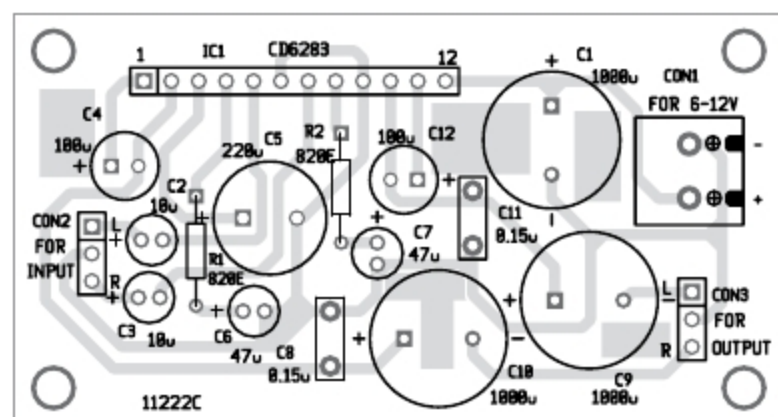


Fig. 3: Components layout for the PCB

PARTS LIST

Semiconductors:

IC1 - CD6283 audio amplifier

Resistors (all 1/4-watt, $\pm 5\%$ carbon):

R1, R2 - 820-ohm

Capacitors:

C1, C9, C10 - 1000 μ F, 25V electrolytic

C2, C3 - 10 μ F, 25V electrolytic

C4, C12 - 100 μ F, 25V electrolytic

C5 - 220 μ F, 25V electrolytic

C6, C7 - 47 μ F, 25V electrolytic

C8, C11 - 0.15 μ F ceramic disk

Miscellaneous:

CON1 - 2-pin terminal connector

CON2, CON3 - 3-pin connector

- 4-ohm, 4W speaker (2 Nos.)

- Suitable heat-sink for IC CD6283

- 6-12V DC regulated power supply

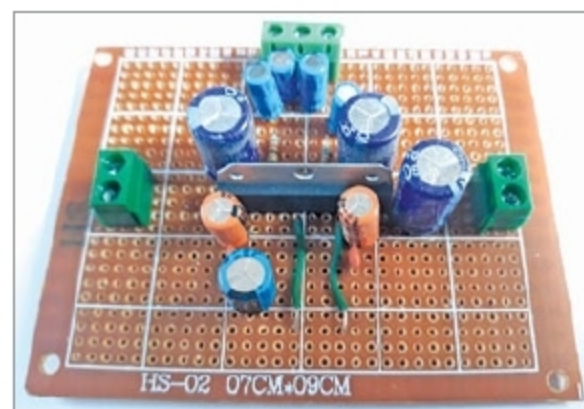


Fig. 4: Author's prototype

nel output via electrolytic capacitor C9. A 4-ohm, 4-watt speaker each is connected at CON3 for left and right channels, respectively.

Construction and testing

An actual-size PCB layout for the amplifier is shown in Fig. 2 and its components layout in Fig. 3. After assembling the circuit on the PCB, connect a 6-12V power supply across CON1.

After completing the wiring, connect left (L) and right (R) stereo audio inputs from a mobile/laptop/desktop at CON2. Then connect the speakers at CON3. Take a 6V or 12V

battery and connect it to the amplifier circuit.

You can calibrate the circuit by connecting a signal generator (set at 1 kHz) to left and right inputs at CON2. You should hear a loud amplified tone from left and right speakers at the output. You can also use an MP3 player instead of signal generator to calibrate the circuit.

Optional 22-kilo-ohm potentiometers can be connected at CON2's left and right inputs for volume control. Your amplifier is ready to use! **EFY**



Raj K. Gorkhali is a hobbyist and a regular contributor to EFY