

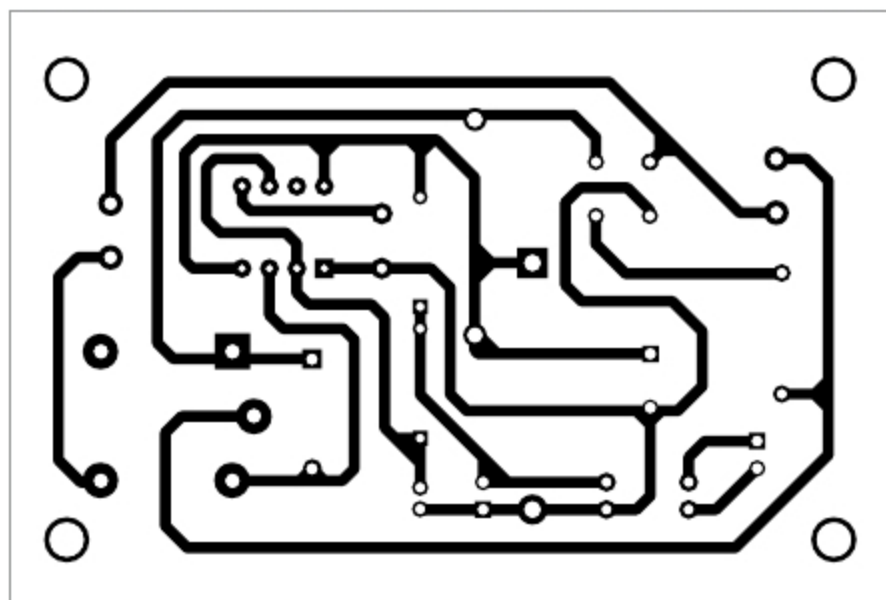


Fig. 3: Actual-size PCB layout for the smart bulb holder

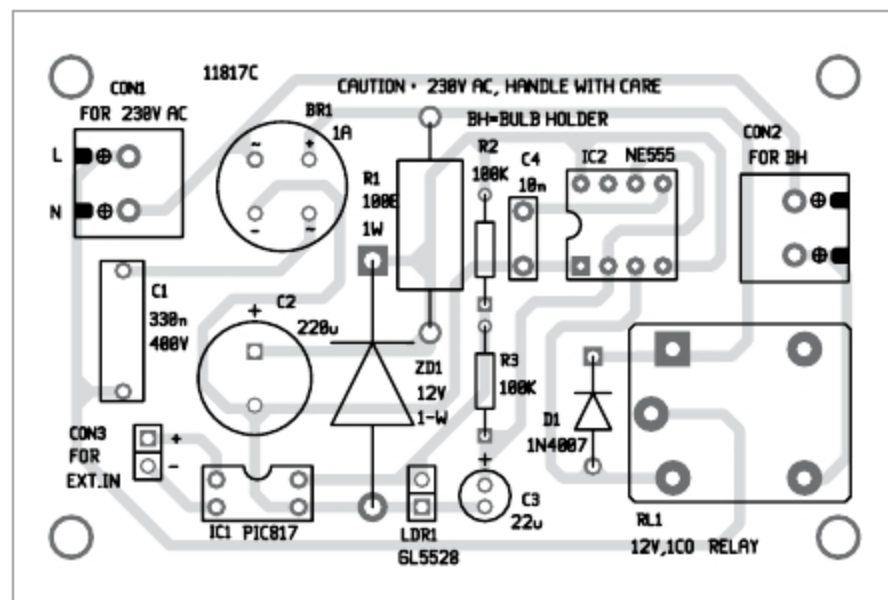


Fig. 4: Components layout of the PCB

PARTS LIST

Semiconductors:

- IC1 - PC817 opto-coupler
- IC2 - NE555 timer
- BR1 - 1A bridge rectifier
- D1 - 1N4007 rectifier diode
- ZD1 - 12V, 1-watt Zener diode

Resistors (all 1/4-watt, $\pm 5\%$ carbon), unless stated otherwise:

- R1 - 100-ohm, 1-watt
- R2, R3 - 100-kilo-ohm

Capacitors:

- C1 - 330nF, 400V ceramic disk
- C2 - 220 μ F, 25V electrolytic
- C3 - 22 μ F, 25V electrolytic
- C4 - 10nF ceramic disk

Miscellaneous:

- CON1, CON2 - 2-pin terminal connector
- CON3 - 2-pin connector
- LDR1 - GL5528 LDR
- RL1 - 12V, single changeover relay
- Bulb holder

As you might notice in the diagram, there's also a galvanically-isolated switch/sensor input in the device built around a common photocoupler PC817 (IC1). The option allows you to remove LDR1 and control the smart bulb holder from an external IoT (or similar) gadget if you desire to have a simple home automation project. It is to be noted here that if the photocoupler is in active state, the bulb will switch off. Needless to say, the photocoupler requires a current-limiter resistor at its input to set the typical forward current close to 20mA at 1.2V typical forward voltage.

Construction and testing

The entire circuit can be assembled on a rectangular piece of perforated or general-purpose PCB (refer author's prototype). An actual-size PCB layout

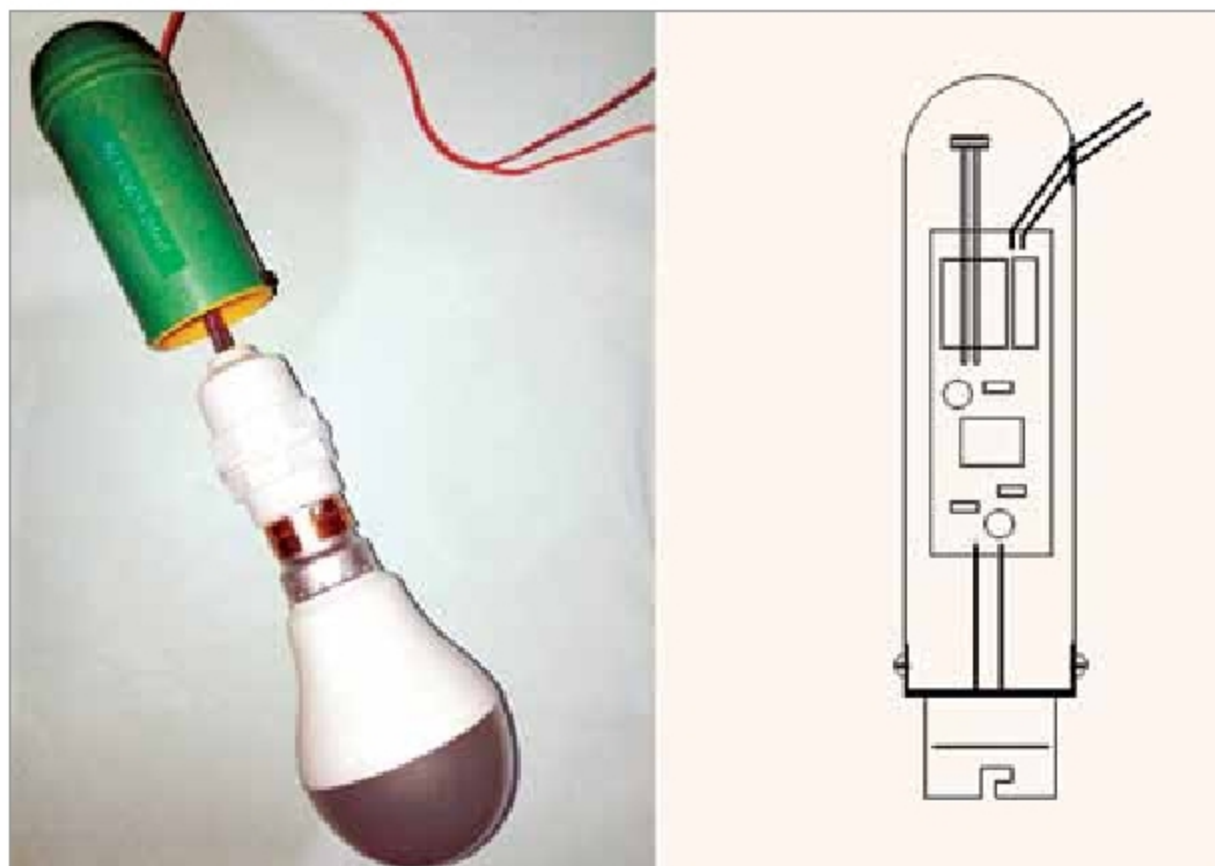


Fig. 5: A sample enclosure layout

for the smart bulb holder is, however, shown in Fig. 3 and its components layout in Fig. 4. After assembling the circuit on the PCB, connect the 230V AC mains across CON1.

A small (waterproof) translucent enclosure is a must for this project. Prototype enclosures come in many shapes and sizes. It would be better to make your own enclosure if you've access to a 3D printer as it'll give your model a polished look. A sample enclosure layout is also depicted here in Fig. 5 for your quick reference.

Author's note. At first, the dimmable daylight LED bulb enclosed prototype was used for performance evaluation. Later, it was mounted on a garden lamp pole, and the real-world results (till now) are very promising.

This smart bulb holder not only works as an energy-saving outdoor light bulb but also serves as a security light bulb or home occupancy indicator to deter prowlers even when you're on a vacation.

Caution. This circuit involves the direct use of 230V AC mains voltage, which is dangerous, and the chances of getting an electric shock are high if not handled properly. If you are not used to handling such voltages, please get the help of a qualified person. **EFY**



T.K. Hareendran is an electronics designer, hardware beta tester, technical author, and product reviewer. He is founder and promoter of TechNode