



THE BEST

CONNECTOR SYSTEMS

FOR HOME APPLIANCES, AUTOMOTIVES AND HVAC



MADE IN GERMANY

Customers India

- BOSCH
- IDEAL BOILERS
- LEONI
- VARROC
- BAJAJ
- DAIMLER
- BENZ
- DHOOT

STOCKO CONTACT GmbH is a World Leading Manufacturer of crimp terminals, Insulation Displacement Connectors and Lighting systems in Automotive, White Goods and HVAC Industries. Stocko has an IN HOUSE Machine Design and Development Centre where Hand Operated to Fully Automatic Machines are built. This increases Efficiency and Reliability on Stocko Parts Worldwide. In India, several OEM's and Harness Makers use Stocko parts for their versatile applications ranging from Automotive to HVAC to Home Appliances markets.

- Wide range of Crimp Terminals, Tabs and Pins
- Multiple IDC Connector Systems from 2.5mm to 5MM
- IDC – Connectors, Machines and Tools • German Design, Precision and Quality
- Over 7.5 Million Connectors Sold in 2017-18

Applications

- Stoves
- Lighting Systems
- Air Conditioners
- Refrigerators
- Washing Machine
- HVAC Industry

www.stocko-contact.com

AURO
CONTROLS
PRIVATE LIMITED
ISO 9001:2008 COMPANY
PUNE, INDIA

Florina Apts., 6th Floor, S.No. 2/1/7 Erandwane, Off. Karve Road,
Pune 411 004. India. Tel.: 020-25465915, Nachiket: +91-8600182797

AUTHORIZED DISTRIBUTORS IN INDIA, SRI LANKA AND UAE

www.aurocontrols.com

PARTS LIST

Semiconductors:

Board1 - Arduino Uno
Board2 - Arduino Pro Mini
IRRX1 - TSOP1738
D1 - 1N4004 rectifier diode
T1 - BC547 npn diode

Resistors (all 1/4-watt, ±5% carbon):

R1 - 4.7-kilo-ohm

Miscellaneous:

CON1 - 2 pin terminal connector
CON2 - 4 pin connector
CON3 - 3 pin connector
- 5V regulated power supply
- Veroboard
- Jumper wires

(All these are available from kitsnspares.com)

tively. That is, if the code received is DBC8CB72, pin 13 will turn on; if the code received is 5A33C754, pin 13 will turn off.

EFY Note
The source code
of this project
is available
for free download
at source.efymag.com

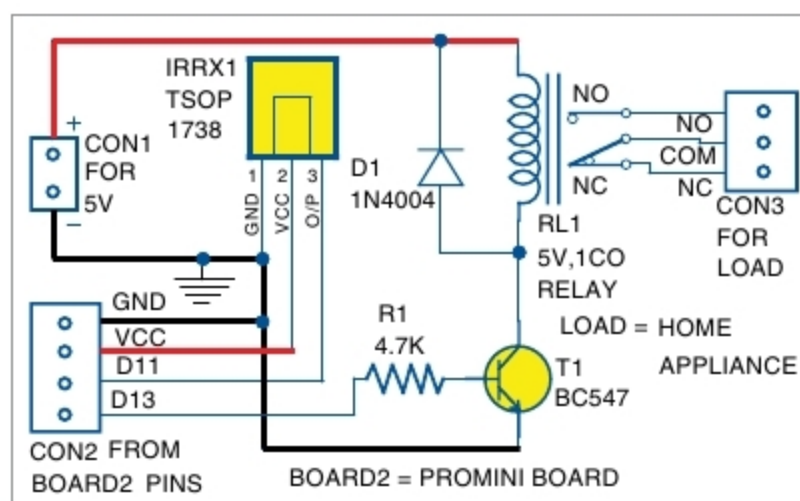


Fig. 5: Circuit diagram for home automation

Home automation circuit

The circuit diagram for home automation is shown in Fig. 5. It is built around Arduino Pro Mini (Board2), IR sensor TSOP1738, npn transistor BC547 (T1), 5V, single-changeover relay (RL1) and a few other components.

After uploading home_auto.ino code to Arduino Pro Mini, connect it to 5V DC power source at connector CON1.

Connect output of TSOP1738 to pin 11 of Pro Mini (Board2). Pin 13 is

used as the output pin to turn on and turn off the appliance by pressing Vol+ and Vol- buttons of the remote controller, respectively. So, connect pin 13 to the base of transistor BC547, which energises 5V relay (RL1).

Employ 1N4004 diode to protect the transistor from back emf flow from the relay coil. A three-pin connector (CON3) may be

used across relay contacts for connecting AC/DC loads or such appliances as lights and fans.

Working of the circuit is simple. After powering on the circuit, press Vol+ button on the remote controller to switch on the home appliance. Press Vol- button on the remote to switch off the home appliance connected to CON3. **EFY**



Shamsudheen Marakkar is pursuing M.Tech in robotics and intelligent systems