



THE BEST CONNECTOR SYSTEMS

FOR HOME APPLIANCES, AUTOMOTIVES AND HVAC


MADE IN GERMANY

Customers India

- BOSCH
- IDEAL BOILERS
- LEONI
- VARROC
- BAJAJ
- DAIMLER
- BENZ
- DHOOT

STOCKO CONTACT GmbH is a World Leading Manufacturer of crimp terminals, Insulation Displacement Connectors and Lighting systems in Automotive, White Goods and HVAC Industries. Stocko has an IN HOUSE Machine Design and Development Centre where Hand Operated to Fully Automatic Machines are built. This increases Efficiency and Reliability on Stocko Parts Worldwide. In India, several OEM's and Harness Makers use Stocko parts for their versatile applications ranging from Automotive to HVAC to Home Appliances markets.

- Wide range of Crimp Terminals, Tabs and Pins
- Multiple IDC Connector Systems from 2.5mm to 5MM
- IDC – Connectors, Machines and Tools • German Design, Precision and Quality
- Over 7.5 Million Connectors Sold in 2017-18

Applications

- Stoves
- Lighting Systems
- Air Conditioners
- Refrigerators
- Washing Machine
- HVAC Industry

www.stocko-contact.com



AURO CONTROLS PRIVATE LIMITED
ISO 9001:2008 COMPANY
PUNE, INDIA



Florina Apts., 6th Floor, S.No. 2/1/7 Erandwane, Off. Karve Road,
Pune 411 004. India. Tel.: 020-25465915, Nachiket: +91-8600182797

AUTHORIZED DISTRIBUTORS IN INDIA, SRI LANKA AND UAE

www.aurocontrols.com

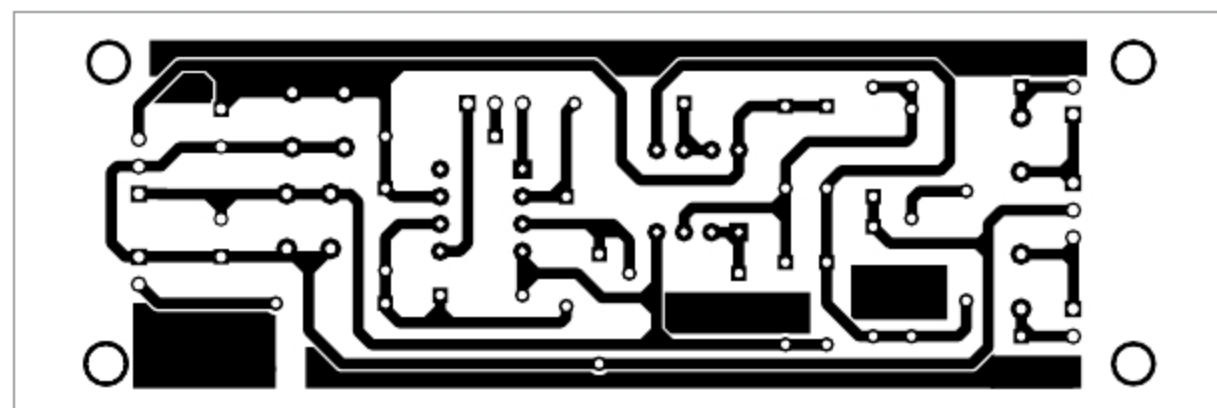


Fig. 2: Actual-size PCB layout of a high impedance differential probe

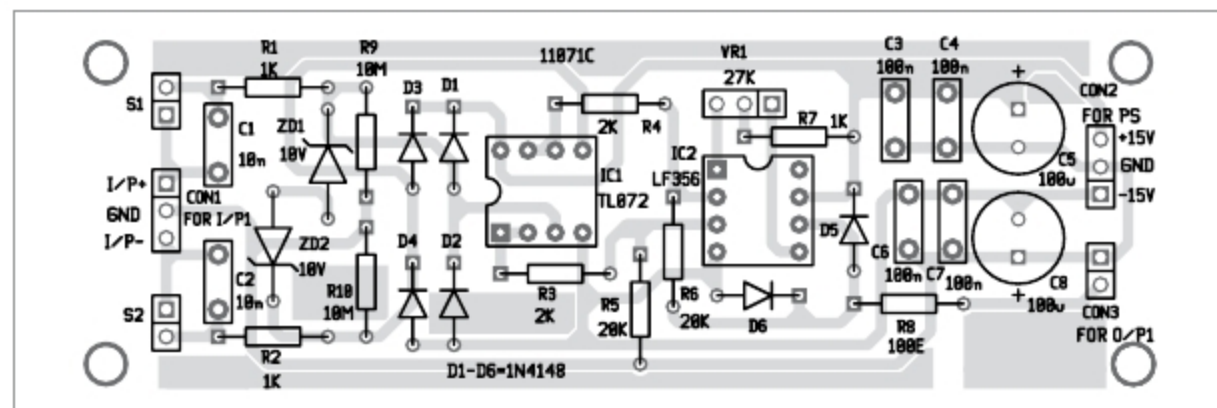


Fig. 3: Components layout of the PCB

and ZD2). The differential voltage of the probe is limited by ZD1 and ZD2 at around 10V. The probe is intended to be used at much lower differential voltages. This is why the IC2 works like a

differential amplifier with a gain of 10. IC2 must have a gain product bandwidth (GBW) several times higher than the GBW of IC1. Or else, the IC2 will limit the bandwidth of

the probe. If LF357 is used instead of LF356, the bandwidth will be greater.

In all the cases stated above, the 3dB bandwidth is above 30kHz. The power supply is at least 12V and preferably $\pm 15V$, and it should be well filtered. If LF356 or LF357 is used, the potentiometer VR1 should be a multi-turn trimmer with a resistance between 22- and 27-kilo-ohm.

Construction and testing

An actual-size PCB layout of a high impedance differential probe is shown in Fig. 2 and its components layout in Fig. 3. Assemble the circuit on the PCB. Connect $\pm 15V$ power supply across CON2 on the PCB.

Depending on the application, use an appropriate connector such as BNC at CON1. **EFY**

Petre Tzv Petrov was a researcher and assistant professor at the Technical University of Sofia, Bulgaria and expert-lecturer in OFPPT (Casablanca), Kingdom of Morocco. Now, he is working as an electronics engineer in the private sector in Bulgaria