

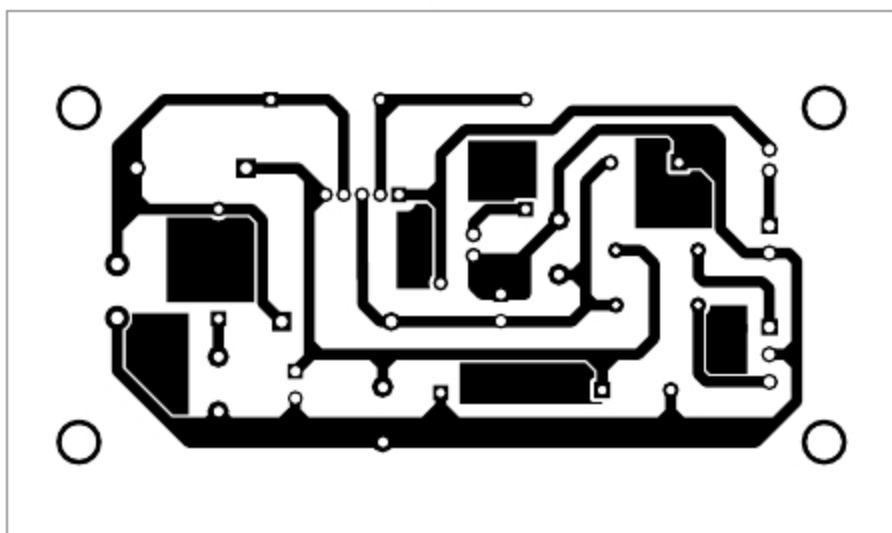


Fig. 3: Actual-size PCB layout of the amplifier

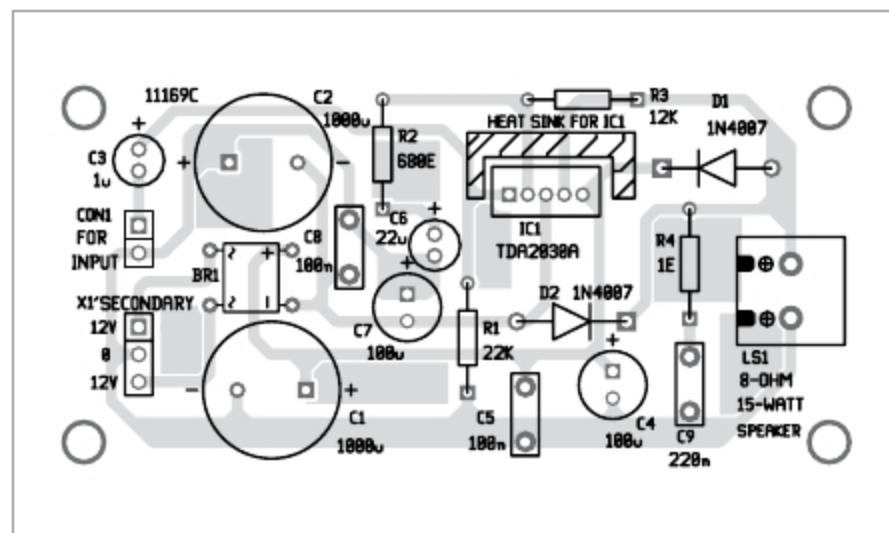


Fig. 4: Components layout of the PCB

laptop/mobile phone across CON1 and the 8-ohm, 15-watt speaker across LS1. Connect the transformer's secondary output (12V-0-12V) to the PCB and its primary to 230V AC mains.

You can also construct your amplifier on veroboard (5cm × 7cm). Mount IC1 in the middle of veroboard. Use a 2-pin connector on the left side and a 3-pin connector on the right side of the veroboard. The 2-pin connector is used for audio

input, and the 3-pin connector is for dual power supply. Solder all the remaining components like resistors, capacitors, diodes, etc, using a low wattage soldering iron. You will need a suitable heat sink for IC1.

After connecting the dual power supply (12V-0-12V) to the circuit, you can test the circuit. For that, take a metal screwdriver and gently touch on the input terminal. You will hear a humming sound from the speaker, which means your amplifier is work-

ing. Note that the output power of amplifier will depend on the power supply.

Connect audio input at CON1 from any audio source such as MP3 player, laptop, or mobile phone. **EFY**




Raj K. Gorkhali is a regular contributor to EFY and an electronics hobbyist

www.efy.in

EFYGROUP
YOURS SINCE 1969

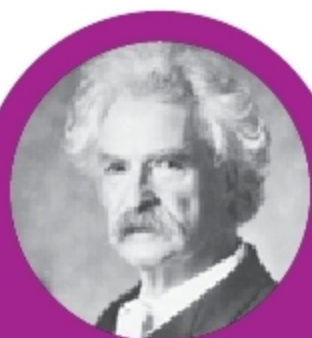“
**Many a small thing has
been made large by the
right kind of advertising.**
”



-Mark Twain

