

Now Book Your Ads Online

And Get

25%

Instant Discount!

ALL CREDIT CARD / DEBIT CARD /
NET BANKING ACCEPTED



You can even
select the position
of your choice.



Facility is
available for
multiple insertions.



Pay online and
get confirmation
of release.

Check out on
www.efymag.com/advertise

Scan this Code

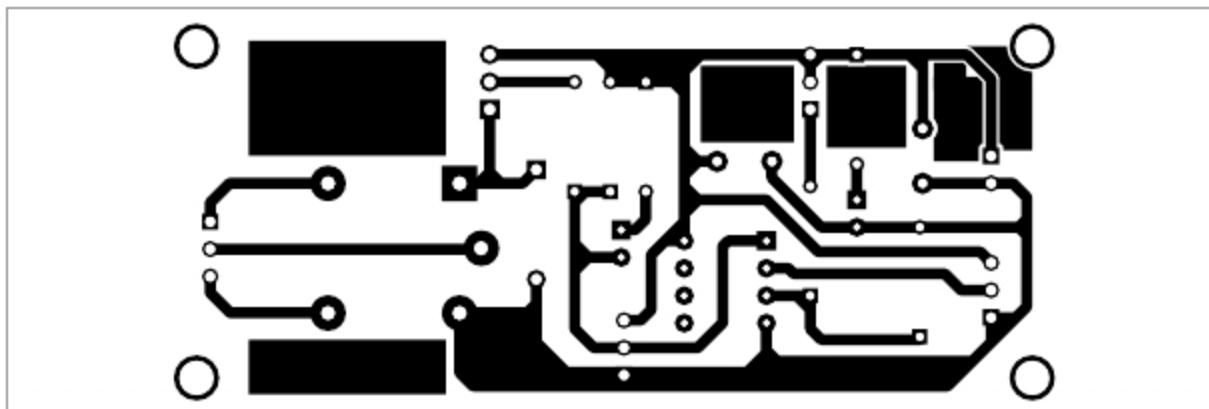


Fig. 4: Actual-size PCB layout of overcurrent fault detector

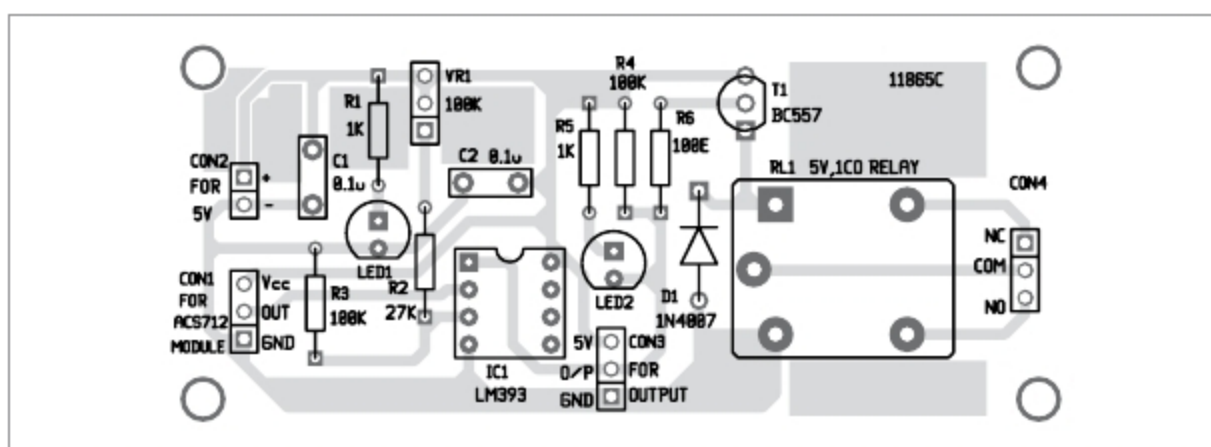


Fig. 5: Components layout of the PCB

like annunciator (or connect/disconnect any electrical device) connected across CON4 once the current reaches a particular level.

Construction and calibration

An actual-size PCB layout for the overcurrent fault detector is shown in Fig. 4 and its components layout in Fig. 5. After assembling the circuit on PCB, connect a 5V across CON2. Connect a 12V battery at IP+ and load at IP- of the ACS712 sensor module.

The trip-point can easily be configured through the potmeter (VR1). The trip-point in the author's prototype is set at 3A.

To set up for a particular application, you can alter the values of VR1 and R2. Assume that you need an overcurrent fault detection just above 2A. At the current of 2A, the ACS712 module roughly gives an output of 2.87V, and the same voltage should be at its inverting input pin. Therefore you should tune VR1 to set the appropriate voltage at the non-inverting input of IC1 so that it provides an overcurrent fault alert signal (logic-low) when the current level goes beyond 2A.

Note. The calibration process demands both theoretical and empirical skills. ACS712 current sensor used here can handle current up to 5A.

PARTS LIST

Semiconductors:

- IC1 - LM393 operational amplifier
- D1 - 1N4007 rectifier diode
- T1 - BC557 pnp transistor
- LED1, LED2 - 5mm LED

Resistors (all 1/4-watt, $\pm 5\%$ carbon):

- R1, R5 - 1-kilo-ohm
- R2 - 27-kilo-ohm
- R3, R4 - 100-kilo-ohm
- R6 - 100-ohm
- VR1 - 100-kilo-ohm potmeter

Capacitors:

- C1, C2 - 0.1 μ F ceramic disk

Miscellaneous:

- CON1, CON3, CON4 - 3 pin terminal connector
- CON2 - 2 pin terminal connector
- RL1 - 5V, single-changeover relay
- ACS712 module (5A)
- 8-pin IC base
- 5V regulated power supply

It can convert input current into an analogue output voltage of about 2.5V plus 185mV/A. One drawback of the ACS712 sensor is that it tends to be quite unstable at lower currents. It is hypersensitive to external magnetic fields, so keep the working circuit away from strong magnetic fields. **EFY**



T.K. Hareendran is an electronics designer, hardware beta tester, technical author, and product reviewer